



Chapter 3

Gate-Level Minimization

J.J. Shann

1



§3-2

1. Simplify the following Boolean function into sum-of-products by using Karnaugh maps (K-maps), and calculate the gate input counts of F before and after the optimization:

(a) i. $F(X, Y, Z) = \Sigma m(1, 3, 4, 5, 6, 7)$

ii. $F(X, Y, Z) = XY + XZ + X'YZ'$

(b) $F(X, Y, Z) = XYZ' + (X' + Z)(Y + Z')$

(a)

X \ YZ	00	01	11	10
0				
1				

X \ YZ	00	01	11	10
0				
1				

EX-2

2

§3-3

2. Optimize the following Boolean function into sum-of-products by using K-map. Find all prime implicants and essential prime implicants, and apply the selection rule:

(a) $F(A, B, C, D) = \Sigma m(1, 5, 6, 7, 11, 12, 13, 14, 15)$

(b) $F(A, B, C, D) = A'BCD + A'BCD' + A'C'D + AB'D + ACD' + ABC + (A + B' + C + D)'$

(a)

CD \ AB	00	01	11	10
00				
01				
11				
10				

EX-3

3

§3-4

3. Optimize the following function into (i) sum-of-products and (ii) product-of-sums forms by using K-map, and calculate the gate input count for each form:

(a) $F(A, B, C, D) = \Sigma m(1, 5, 6, 7, 11, 12, 13, 14, 15)$

(b) $F(A, B, C, D) = A'BCD + A'BCD' + A'C'D + AB'D + ACD' + ABC + (A + B' + C + D)'$

(a)

CD \ AB	00	01	11	10
00				
01				
11				
10				

CD \ AB	00	01	11	10
00				
01				
11				
10				

EX-4

4



§3-5

4. Optimize the following Boolean function F together with don't-care condition d into (i) sum-of-products and (ii) product-of-sums forms by using K-map. Express each simplified function in " Σm " notation, and determine the gate input count of it.

(a) $F(W, X, Y, Z) = \Sigma m(5, 7, 11, 14, 15),$

$d(W, X, Y, Z) = \Sigma m(1, 6, 12, 13)$

(b) $F(W, X, Y, Z) = \Sigma m(0, 2, 5, 8, 14, 15),$

$d(W, X, Y, Z) = \Sigma m(4, 7, 10, 13)$

(a)

WX \ YZ				
	00	01	11	10
00				
01				
11				
10				

WX \ YZ				
	00	01	11	10
00				
01				
11				
10				

EX-5

5



Quine-McCluskey Method

5. Optimize the following Boolean function F together with don't-care condition d by using Quine-McCluskey method.

(a) $F(X, Y, Z) = \Sigma m(1, 5, 6), d(X, Y, Z) = \Sigma m(2, 7)$

(b) i. $F(W, X, Y, Z) = \Sigma m(5, 7, 11, 14, 15),$

$d(W, X, Y, Z) = \Sigma m(1, 6, 12, 13)$

ii. $F(W, X, Y, Z) = \Sigma m(0, 2, 5, 8, 14, 15),$

$d(W, X, Y, Z) = \Sigma m(4, 7, 10, 13)$

(a)

Implication Table		
Column 1	Column 2	Column 3

Implication Chart



EX-6

6

Multiple-Level Circuit Optimization

6. Use decomposition to find a minimum gate input count, multiple-level implementation for each of the following functions using AND and OR gates and inverters. Draw the logic diagram and calculate the gate input counts of F before and after the decomposition.

(a) $F(A, B, C, D) = ABC' + A'BC + A'CD + AC'D$

(b) $F(A, B, C, D) = AC + BC + A'BD + AB'D$

EX-7

7

§3-6

7. Simplify the Boolean function and implement it

(a) $F(A, B, C) = \Sigma m(1, 3, 4, 5, 6)$

i. by 2-level NAND gates ii. by 2-level NOR gates

(b) $F(A, B, C, D) = \Sigma m(1, 5, 6, 7, 11, 12, 13, 14, 15)$

i. by 2-level NAND gates ii. by 2-level NOR gates

(a)

A	BC			
	00	01	11	10
0				
1				

A	BC			
	00	01	11	10
0				
1				

EX-8

8

§3-7

8. Simplify the following functions with AND-NOR, NAND-AND, OR-NAND, NOR-OR 2-level forms:

(a) $F(A, B, C) = \Sigma m(1, 3, 4, 5, 6)$

(b) $F(A, B, C, D) = \Sigma m(1, 5, 6, 7, 11, 12, 13, 14, 15)$

(a)

A \ BC	BC			
	00	01	11	10
0				
1				

A \ BC	BC			
	00	01	11	10
0				
1				

EX-9

9

§3-8

9. Consider a 3-bit message to be transmitted together w/ an odd parity bit. Design the odd-parity generation function P for the transmitter and the odd-parity checking function C for the receiver. Assume that the output of the checker is equal to 1 if error occurs.

EX-10

10

Brief Answers of the Exercises (1/4)

1. (a) i. $X + Z$, $GIC_{after} = 2$
 ii. $XZ + YZ'$, $GIC_{before} = 12$, $GIC_{after} = 7$
 (b) $Y + X'Z'$, $GIC_{before} = 13$, $GIC_{after} = 6$
2. (a) PIs: BD, AB, BC, ACD, A'C'D ; EPIs: AB, BC, ACD, A'C'D
 $F = AB + BC + ACD + A'C'D$
 (b) PIs: A'B, AC, BC, A'C'D, AB'D, B'C'D ; EPIs: A'B, AC
 $F = A'B + AC + B'C'D$
3. (a) $F = AB + BC + ACD + A'C'D$, $GIC = 16$;
 $F = (B+D)(A'+B+C)(A+B+C')(A+C+D)$, $GIC = 17$
 (b) $F = A'B + AC + B'C'D$, $GIC = 13$
 $F = (A'+B'+C)(A+B+C')(B+C+D)$, $GIC = 15$

EX-11

11

Brief Answers of the Exercises (2/4)

4. (a) i. $F = WYZ + XZ + \begin{Bmatrix} WX \\ XY \end{Bmatrix} = \Sigma m(5, 7, 11, 12, 13, 14, 15)$, $GIC = 10$
 $\begin{Bmatrix} WX \\ XY \end{Bmatrix} = \Sigma m(5, 6, 7, 11, 13, 14, 15)$, $GIC = 10$
 ii. $F = (X+Z)(W+X) \begin{Bmatrix} (Y+Z) \\ (W+Z) \end{Bmatrix} \begin{Bmatrix} (W'+Y) \\ (X+Y) \end{Bmatrix}$ * 4 possible solutions
- (b) i. $F = X'Z' + XZ + \begin{Bmatrix} WXY \\ WYZ' \end{Bmatrix} = \Sigma m(0, 2, 5, 7, 8, 10, 13, 14, 15)$, $GIC = 12$
 $\begin{Bmatrix} WXY \\ WYZ' \end{Bmatrix} = \Sigma m(0, 2, 5, 7, 8, 10, 13, 14, 15)$, $GIC = 12$
 ii. $F = (X+Z') \begin{Bmatrix} (W'+X'+Y) \\ (X'+Y+Z) \end{Bmatrix} \begin{Bmatrix} (W+X'+Z) \\ (W+X'+Y') \end{Bmatrix}$ * 4 possible solutions
5. (a) $F = Y'Z + \begin{Bmatrix} YZ' \\ XY \end{Bmatrix}$
 (b) i. $F = WYZ + XZ + \begin{Bmatrix} XY \\ WX \end{Bmatrix}$
 ii. $F = X'Z' + XZ + \begin{Bmatrix} WXY \\ WYZ' \end{Bmatrix}$

EX-12

12

Brief Answers of the Exercises (3/4)

6. (a) $F = (B + D) (AC' + A'C)$, $GIC_{\text{before}} = 18$, $GIC_{\text{after}} = 12$

(b) $F = (A + B) (C + D (A' + B'))$ or
 $= (A + B) (C + D) (C + A' + B')$
 $GIC_{\text{before}} = 16$, $GIC_{\text{after}} = 12$

7. (a) i. $F = A'C + AC' + \begin{Bmatrix} AB' \\ B'C \end{Bmatrix}$
 $= ((A'C)' (AC')' \begin{Bmatrix} (AB')' \\ (B'C)' \end{Bmatrix})'$

ii. $F = (A+C)(A'+B'+C')$
 $= ((A+C)' + (A'+B'+C')')$

(b) i. $F = AB + BC + ACD + A'C'D$
 $= ((AB)'(BC)'(ACD)'(A'C'D)')$

ii. $F = (B+D) (A'+B+C) (A+B+C') (A+C+D)$
 $= ((B+D)' + (A'+B+C)' + (A+B+C')' + (A+C+D)')$

EX-13

13

Brief Answers of the Exercises (4/4)

8. (a) AND-NOR, NAND-AND: AOI

$$F' = A'C' + ABC$$

$$F = (A'C')' (ABC)'$$

OR-NAND, NOR-OR: OAI

$$F' = (A'+C)(A+C') \begin{Bmatrix} (A'+B) \\ (B+C') \end{Bmatrix}$$

$$F = (A'+C)' + (A+C')' + \begin{Bmatrix} (A'+B)' \\ (B+C')' \end{Bmatrix}$$

(b) AND-NOR, NAND-AND: AOI

$$F' = B'D' + AB'C' + A'B'C + A'C'D'$$

$$F = (B'D')' (AB'C')' (A'B'C)' (A'C'D')'$$

OR-NAND, NOR-OR: OAI

$$F' = (A'+B') (B'+C') (A'+C'+D') (A+C+D')$$

$$F = (A'+B')' + (B'+C')' + (A'+C'+D')' + (A+C+D)'$$

9. $P = (x \oplus y \oplus z)'$, $C = (x \oplus y \oplus z \oplus P)'$

EX-14

14