

Chapter 2

Boolean Algebra and Logic Gates

J.J. Shann

■1


Chapter Overview

- 2-1 Introduction
- 2-2 Basic Definitions
- 2-3 Axiomatic Definition of Boolean Algebra
- 2-4 Basic Theorems and Properties of Boolean Algebra
- 2-5 Boolean Functions
- 2-6 Canonical and Standard Forms
- 2-7 Other Logic Operations
- 2-8 Digital Logic Gates
- 2-9 Integrated Circuits
- 補充資料：Technology Parameters

Standard form	Non-Standard form
Canonical form	

J.J. Shann 2-2

■2

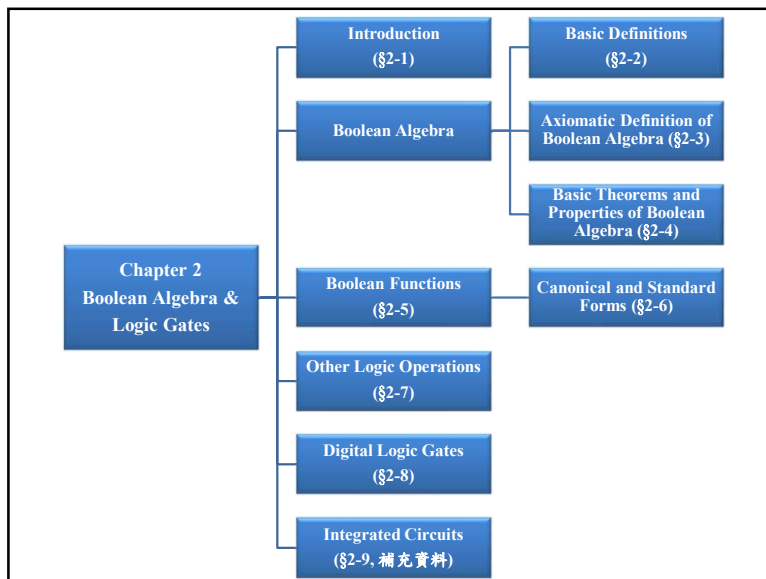

■3

Exercises in Textbook (6th ed.)

Sections	Exercises	Typical Ones
§2-3	2.1	2.1(a)
§2-4	2.2~2.4, 2.24	2.3, 2.4
§2-5	2.5~2.9, 2-13	2.6
§2-6	2.10, 2.11, 2.15~2.23, 2.27, 2.29~2.31	2.17(a)*, 2.20, 2.22*, 2.30
§2-7	2.12, 2.14, 2.25	2.14, 2.25
§2-8	2.26, 2.28, 2.32, 2.33	2.28, 2.32*

* : Answers to problems appear at the end of the text.

J.J. Shann 2-4

■4

2-1

Introduction

J.J. Shann

■5

Introduction

- Important factor of digital circuit design:
 - the **cost** of the circuit
- ⇒ Find **simpler** and **cheaper**, but **equivalent**, realizations of a circuit.
- **Boolean algebra:**
 - Mathematical methods that simplify circuits rely primarily on Boolean algebra.

J.J. Shann 2-6

■6

2-2

Basic Definitions

J.J. Shann

■7

Basic Definitions

- A **deductive mathematical system** may be defined with
 - a set of **elements**: S
 - a set of **operators**: binary/unary operator
 - a number of unproven **axioms** or **postulates**:
 - Form the basic assumptions from which it is possible to deduce the **rules**, **theorems**, and **properties** of the system

J.J. Shann 2-8

■8

Common Postulates

- elements: $\in S$
- operators
- axioms or postulates

■ For algebraic structures:

1. **Closure**
 - E.g.: the set of natural numbers $N = \{1, 2, 3, 4, \dots\}$ is closed w.r.t. “+” (arithmetic addition), but not to “−” (arithmetic subtraction)
2. **Associative law:** $(x * y) * z = x * (y * z)$
3. **Commutative law:** $x * y = y * x$
4. **Identity element:** $e, e * x = x * e = x$
 - E.g.: 0 is an identity element w.r.t. “+” on the set of integers $I = \{\dots, -3, -2, -1, 0, 1, 2, 3, \dots\}$
5. **Inverse:** $x * y = e$
 - E.g.: In the set of integers, I , and the operator $+$, with $e = 0$, the inverse of an element a is $(-a)$.
6. **Distributive law:** $x * (y \cdot z) = (x * y) \cdot (x * z)$

J.J. Shann 2-9

■9

2-3


Axiomatic Definition of Boolean Algebra

J.J. Shann

■10

Axiomatic Definition of Boolean Algebra

 - 1854 George Boole: Boolean algebra
- 1904 E. V. Huntington: postulates https://en.wikipedia.org/wiki/Edward_Vernilyle_Huntington
- 1938 C. E. Shannon: 2-valued Boolean algebra (switching algebra, binary logic)



George Boole
(1815~1864)

https://en.wikipedia.org/wiki/George_Boole



C.E. Shannon
(1916~2001)

https://en.wikipedia.org/wiki/Claude_Shannon

J.J. Shann 2-11

■11

Boolean Algebra

- Boolean algebra: an algebra structure
 - a set of elements: B
 - a set of operators: 2 binary operators: $+$, \cdot
 - (Huntington) postulates

J.J. Shann 2-12

■12

Huntington Postulates

(Huntington) postulates:

- (a) Closure w.r.t the operator $+$.
(b) Closure w.r.t the operator \cdot .
- (a) An identity element w.r.t. $+$: $0, x + 0 = 0 + x = x$
(b) An identity element w.r.t. \cdot : $1, x \cdot 1 = 1 \cdot x = x$
- (a) Commutative w.r.t. $+$: $x + y = y + x$
(b) Commutative w.r.t. \cdot : $x \cdot y = y \cdot x$
- (a) \cdot is distributive over $+$: $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$
(b) $+$ is distributive over \cdot : $x + (y \cdot z) = (x + y) \cdot (x + z)$
- Complement: x' , (a) $x + x' = 1$ (b) $x \cdot x' = 0$
- There exists at least two elements $x, y \in B$ s.t. $x \neq y$.

❖ **Associative law**: can be derived from the other postulates

J.J. Shann 2-13

■13

Two-Valued Boolean Algebra

- Set of elements: $B = \{0, 1\}$
- Set of operators: 2 binary operators: $+, \cdot$

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

AND

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

OR

x	x'
0	1
1	0

NOT

(Postulate 5)

- (Huntington) postulates:

J.J. Shann 2-14

■14

(Huntington) postulates:

- Closure
- Identity elements: two; 0 for $+$, 1 for \cdot
 $x + 0 = 0 + x = x, x \cdot 1 = 1 \cdot x = x$
- Commutative laws: $x + y = y + x, x \cdot y = y \cdot x$
- (a) \cdot is distributive over $+$: $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$
(b) $+$ is distributive over \cdot : $x + (y \cdot z) = (x + y) \cdot (x + z)$
- Complement:
(a) $x + x' = 1: 0 + 0' = 0 + 1 = 1, 1 + 1' = 1 + 0 = 1$
(b) $x \cdot x' = 0: 0 \cdot 0' = 0 \cdot 1 = 0, 1 \cdot 1' = 1 \cdot 0 = 0$
- $B = \{0, 1\}, 0 \neq 1$.

J.J. Shann 2-15

■15

Proof by Truth Table

* **Prove 4(b)!**

<Proof> 4(a) $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$

x	y	z	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

■16

2-4

Basic Theorems and Properties of Boolean Algebra

J.J. Shann

■17

Basic Theorems and Properties of Boolean Algebra

■ Duality:

- Every algebraic expression deducible from the postulates of Boolean algebra (or truth table) remains valid if the **operators** and **identity elements** are interchanged (OR \leftrightarrow AND, 0 \leftrightarrow 1)

* Positive vs. Negative Logic (p.2-86~2-88)

- E.g.:

$$4.(a) x \cdot (y + z) = (x \cdot y) + (x \cdot z) \quad (b) x + (y \cdot z) = (x + y) \cdot (x + z) \quad \text{dual}$$

$$5.(a) x + x' = 1 \quad (b) x \cdot x' = 0 \quad \text{dual}$$

J.J. Shann 2-18

■18

A. Basic Theorems

■ Postulates and theorems of Boolean algebra:

- Postulates: basic axioms, need no proof
- Theorems: must be proven
 - From the **postulates** and **proven theorems**
 - From **truth table**

J.J. Shann 2-19

■19

dual

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 5, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x + (yz) = (x + y)(x + z)$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

J.J. Shann 2-20

■20

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 5, complement	$x + x' = 1$	$x \cdot x' = 0$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(yz) = (xy)(xz)$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

J.J. Shann 2-21

21

Theorem 1

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 5, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(yz) = (xy)(xz)$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

■ 1(a): $x + x = x$

$$\begin{aligned}
 x + x &= (x + x) \cdot 1 \\
 &= (x + x)(x + x') \\
 &= x + xx' \\
 &= x + 0 \\
 &= x
 \end{aligned}$$

by postulate: 2(b)

x	x + x
0	
1	

5(a)
4(b)
5(b)
2(a)

■ 1(b): $x \cdot x = x$

$$\begin{aligned}
 x \cdot x &= x x + 0 \\
 &= x x + x x' \\
 &= x(x + x') \\
 &= x \cdot 1 \\
 &= x
 \end{aligned}$$

by postulate: 2(a)

x	x · x
0	0 · 0 = 0
1	1 · 1 = 1

5(b)
4(a)
5(a)
2(b)

J.J. Shann 2-22

22

Theorem 2

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 5, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(yz) = (xy)(xz)$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

■ 2(a): $x + 1 = 1$

$$\begin{aligned}
 x + 1 &= 1 \cdot (x + 1) \\
 &= (x + x')(x + 1) \\
 &= x + x' \cdot 1 \\
 &= x + x' \\
 &= 1
 \end{aligned}$$

by postulate: 2(b), 3(b)

x	x + 1
0	
1	

5(a)
4(b)
2(b)
5(a)

■ 2(b): $x \cdot 0 = 0$

$x + 1 = 1$ is proven

↓ by duality principle (OR ↔ AND, 0 ↔ 1)

$x \cdot 0 = 0$

J.J. Shann 2-23

23

Theorem 3: Involution

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 5, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(yz) = (xy)(xz)$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

■ $(x')' = x$

- Postulate 5 defines the complement of x:

$$x + x' = 1 \quad \text{and} \quad x x' = 0$$
- The complement of x' is x and is also $(x')'$.
Since the complement is unique $\Rightarrow (x')' = x$.

x	x'	(x')'
0		
1		

J.J. Shann 2-24

24

Theorem 5: DeMorgan

- 5(a): $(x + y)' = x' y'$

x	y	x + y	(x + y)'	x'	y'	x' y'
0	0					
0	1					
1	0					
1	1					

- 5(b): $(x y)' = x' + y'$

* Prove Theorem 5 by using Postulate 5!

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 3, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$x y = y x$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

25

- Two variables: $(x + y)' = x' y'$, $(x y)' = x' + y'$
- Three or more variables:

$(A + B + C)' = (A + X)'$
 $= A' X'$
 $= A' (B + C)'$
 $= A' (B' C')$
 $= A' B' C'$

let $B + C = X$
by DeMorgan's
substitute $B + C = X$
by DeMorgan's
associative

- Generalized form:

$(A + B + C + \dots + G)' = A' B' C' \dots G'$
 $(A B C \dots G)' = A' + B' + C' + \dots + G'$
 \Rightarrow AND \leftrightarrow OR and complement each literal

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 3, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$x y = y x$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

26

Theorem 6: Absorption

- 6(a): $x + xy = x$

i. $x + xy = x \cdot 1 + xy$
 $= x(1 + y)$
 $= x(y + 1)$
 $= x \cdot 1$
 $= x$

by postulate: 2(b)
4(a)
3(a)
(Theorem) 2(a)
2(b)

ii. Truth table:

x	y	xy	x + xy
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 3, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$x y = y x$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

27

- 6(a): $x + xy = x$

- * Venn diagram:

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 3, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$x y = y x$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(y \cdot z) = (x \cdot y) \cdot z$
Theorem 5, DeMorgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

28

Theorem * : Consensus

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 3, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(yz) = (xy)z$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Theorem 5, DeMorgan	$(x + y)' = x'y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

$$xy + x'z + yz = xy + x'z$$

$$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$$

$$\begin{aligned}
 & xy + x'z + yz \\
 &= xy + x'z + (x + x')yz \quad \dots \text{P2(b), P3(b), P5(a)} \\
 &= xy + x'z + xyz + x'y z \quad \dots \text{P4(a)} \\
 &= xy(1 + z) + x'z(1 + y) \quad \dots \text{P3(a), P4(a)} \\
 &= xy + x'z \quad \dots \text{T2(a), P2(b)}
 \end{aligned}$$

- can be used to **eliminate** redundant terms from Boolean expressions.
- can be used to **generate** redundant terms for further simplification.


* Venn diagram

J.J. Shann 2-29

■29

$$xy + x'z + yz = xy + x'z$$

* Venn diagram:

 

J.J. Shann 2-30

■30

B. Operator Precedence

- Operator precedence for evaluating Boolean expression:

- parenthesis
- NOT
- AND
- OR

- Example:

$$(x + y)' + x'y$$

J.J. Shann 2-31

■31

2-5

Boolean Functions

J.J. Shann

■32

Boolean Functions

■ Boolean algebra:

- is an algebra dealing w/ **binary variables** and **logic ops**
 - binary variables: are designated by letters of the alphabet
 - logic ops: AND, OR, NOT

■ Boolean expression:

- an algebraic expression formed by using
 - binary variables,
 - the constants 0 and 1,
 - the logic op symbols, and
 - parentheses.
- E.g.: $X \cdot (\bar{Y} + Z) + Z \cdot 1$

J.J. Shann 2-33

■33

Boolean Function

■ Boolean function:

- can be described by
 - a **Boolean equation**,
 - a **truth table**, or
 - a **logic ckt diagram**

J.J. Shann 2-34

■34

Boolean Equation

■ Boolean equation:

- consists of a **binary variable** identifying the function followed by an **equal sign** and a **Boolean expression**.
- expresses the logical relationship b/t binary variables
- can be expressed in a variety of ways
 - * **Obtain a simpler expression for the same function.**
- E.g.:

$$F(W, X, Y, Z) = XY\bar{Z} + \bar{Y}Z + \bar{W}XYZ + WXY + \bar{W}XY\bar{Z}$$

$$= X + \bar{Y}Z$$

terms

J.J. Shann 2-35

■35

Truth Table

■ Truth table for a function: is unique

- a list of all combinations of 1's and 0's that can be assigned to the binary variables and a list that shows the value of the function for each binary combination.

- E.g.:

$$F(X, Y, Z) = X + \bar{Y}Z$$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

J.J. Shann 2-36


■36

Logic Circuit Diagram

Logic circuit diagram:

- An algebraic expression for a Boolean function
 \Rightarrow A ckt diagram composed of logic gates
- Circuit **gates** are interconnected by **wires** that carry logic signals.

E.g.: $F(x, y, z) = x + \bar{y}z$

 

* Combinational logic circuits

J.J. Shann 2-37

■37

Example



Present a set of requirements under which an insurance policy will be issued:

The applicant must be

- a married female 25 years old or over, or
- a female under 25, or
- a married male under 25 who has not been involved in a car accident, or
- a married male who has been involved in a car accident, or
- a married male 25 years or over who has not been involved in a car accident.

J.J. Shann 2-38

■38

<Ans.>



Define input variables: 4; w, x, y, z

- $w = 1$ if applicant has been involved in a car accident
- $x = 1$ if applicant is married
- $y = 1$ if applicant is a male
- $z = 1$ if applicant is under 25

Find a Boolean expression which assumes the value 1 whenever the policy should be issued:

- $x y' z'$ 1. a married female 25 years old or over
- $y' z$ 2. a female under 25
- $w' x y z$ 3. a married male under 25 who has not been involved in a car accident
- $w x y$ 4. a married male who has been involved in a car accident
- $w' x y z'$ 5. a married male 25 years or over who has not been involved in a car accident

$\Rightarrow F = x y' z' + y' z + w' x y z + w x y + w' x y z'$ J.J. Shann 2-39

■39

Simplify the expression and suggest a simpler set of requirements:

$$F = x y' z' + y' z + \frac{w' x y z + w x y + w' x y z'}{x y} = x + y' z$$

Insurance policy

- $w = 1$ if applicant has been involved in a car accident
- $x = 1$ if applicant is married
- $y = 1$ if applicant is a male
- $z = 1$ if applicant is under 25

The applicant must be

- married or
- a female under 25.

J.J. Shann 2-40

■40

Inputs → Insurance Policy → Output

Draw the logic circuit diagram:

$$F = x y' z' + y' z + w' x y z + w x y + w' x y z'$$

$= x + y' z$

J.J. Shann 2-41

41

Simplification of Boolean Functions

Boolean algebra is a useful tool for simplifying digital cks.

E.g.:

$$F_2 = x'y'z + x'yz + xy'$$

$$= x'z(y' + y) + xy' \quad \dots \text{Postulate 4(a)}$$

$$= x'z \cdot 1 + xy' \quad \dots \text{Postulate 5(a)}$$

$$= x'z + xy' \quad \dots \text{Postulate 2(b)}$$

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 5, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(yz) = (xy)z$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Theorem 5, DeMorgan	$(x + y)' = x'y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem 7, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

J.J. Shann 2-42

42

$F_2 = x'y'z + x'yz + xy' \dots (a)$

$= x'z + xy' \dots (b)$

$F_2 = x'y'z + x'yz + xy'$

$F_2 = x'z + xy'$

x	y	z	F_2
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

J.J. Shann 2-43

43

A. Algebraic Manipulation

Implementation of Boolean function w/ gates:

- each **term** is implemented w/ a **gate**
- each **literal** designates an **input** to a gate
 - literal*: a primed or unprimed variable
- E.g.: $F_2 = x'y'z + x'yz + xy' \dots 3 \text{ terms \& 8 literal}$
 $= x'z + xy' \dots 2 \text{ terms \& 4 literals}$

Criterion of equipment minimization:

- Minimize the # of "**literals**"
- Minimize the # of "**terms**"

Algebraic manipulation: **literal** minimization

- Method: **cut-and-try** (hard)
 - employ the postulates, basic theorem, ...

J.J. Shann 2-44

44

Example 2-1

- Simplify the following Boolean functions to a minimum # of literals:

$$\begin{aligned} 1. & x(x' + y) \\ &= xx' + xy \\ &= 0 + xy \\ &= xy \quad 3 \rightarrow 2 \end{aligned}$$

$$\begin{aligned} 2. & x + x'y \\ &= (x + x')(x + y) \\ &= 1(x + y) \\ &= x + y \quad 3 \rightarrow 2 \text{ (or by duality from 1)} \end{aligned}$$

Postulate/Theorem	(a)	(b)
Postulate 2, identity element	$x + 0 = x$	$x \cdot 1 = x$
Postulate 5, complement	$x + x' = 1$	$x \cdot x' = 0$
Postulate 3, commutative	$x + y = y + x$	$xy = yx$
Postulate 4, distributive	$x(y + z) = xy + xz$	$x(yz) = (xy)z$
Theorem 1	$x + x = x$	$x \cdot x = x$
Theorem 2	$x + 1 = 1$	$x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Theorem 4, associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
Theorem 5, DeMorgan	$(x + y)' = x'y'$	$(xy)' = x' + y'$
Theorem 6, absorption	$x + xy = x$	$x(x + y) = x$
Theorem *, consensus	$xy + x'z + yz = xy + x'z$	$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$

J.J. Shann 2-45

45

B. Complement of a Function

- Complement of a function F:
 - E.g.: p.2-38 (Insurance Policy)
 - $F = 1$ whenever the insurance policy should be issued
 - $\Rightarrow G = F' = 1$ whenever the insurance policy should **not** be issued
 - interchange of 1's to 0's and 0's to 1's for the values of F in the **truth table**
 - can be derived algebraically by applying **DeMorgan's theorem** \Rightarrow interchange AND and OR ops and complement each variable and constant

$\overline{X + Y} = \overline{X} \cdot \overline{Y}$

$\overline{X \cdot Y} = \overline{X} + \overline{Y}$
 - take the **dual** ($\text{OR} \leftrightarrow \text{AND}$, $0 \leftrightarrow 1$) of the function eq & complement each literal

J.J. Shann 2-47

47

Example 2.2

$\overline{X + Y} = \overline{X} \cdot \overline{Y}$

$\overline{X \cdot Y} = \overline{X} + \overline{Y}$

- Complementing functions by applying DeMorgan's theorem:

E.g.s:

$$\begin{aligned} F_1 &= \overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z & \overline{F}_1 &= (\overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z)' \\ & & &= (\overline{X}Y\overline{Z})' \cdot (\overline{X}\overline{Y}Z)' \\ & & &= (X + \overline{Y} + Z) \cdot (X + Y + \overline{Z}) \end{aligned}$$

$$\begin{aligned} F_2 &= X(\overline{Y}\overline{Z} + YZ) & \overline{F}_2 &= (X(\overline{Y}\overline{Z} + YZ))' \\ & & &= \overline{X} + (\overline{Y}\overline{Z} + YZ)' \\ & & &= \overline{X} + (\overline{Y}\overline{Z})' \cdot (YZ)' \\ & & &= \overline{X} + (Y + Z) \cdot (\overline{Y} + \overline{Z}) \end{aligned}$$

Shann 2-48

48

Example 2.3

Complementing functions by using duals:

- E.g.s: (dual: OR \leftrightarrow AND, 0 \leftrightarrow 1)

$$F_1 = \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z$$

$$\text{dual of } F_1 \Rightarrow (\bar{X} + Y + \bar{Z}) \cdot (\bar{X} + \bar{Y} + Z)$$

$$\begin{aligned} \text{complement each literal} &\Rightarrow (X + \bar{Y} + Z) \cdot (X + Y + \bar{Z}) \\ &= \bar{F}_1 \end{aligned}$$

$$F_2 = X(\bar{Y}\bar{Z} + YZ)$$

$$\text{dual of } F_2 \Rightarrow X + (\bar{Y} + \bar{Z}) \cdot (Y + Z)$$

$$\begin{aligned} \text{complement each literal} &\Rightarrow \bar{X} + (Y + Z) \cdot (\bar{Y} + \bar{Z}) \\ &= \bar{F}_2 \end{aligned}$$

J.J. Shann 2-49

■49

2-6

Canonical & Standard Forms

J.J. Shann

■50

Canonical & Standard Forms

Boolean expressions:

- an expression formed w/:
 - binary variables
 - constants 0 and 1
 - binary operators OR and AND
 - unary operator NOT
 - parentheses
 - equal sign
- Special forms:
 - Canonical forms
 - Standard forms

Boolean expressions

Standard form	Non-Standard form
Canonical form	

J.J. Shann 2-51

■51

A. Canonical Forms

Canonical forms:

- special forms of Boolean expression being expressed directly from **truth tables**
- Two types:
 - sum-of-minterms form*
(minterm) + ... + (minterm)
 - product-of-maxterms form*
(maxterm) • ... • (maxterm)

x	y	z	F_2
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

J.J. Shann 2-52

■52

minterms

- **minterm**: standard product, m_j
 - an **AND** term of the n variables, w/ each variable being **primed** if the corresponding bit is **0** and **unprimed** if a **1**.
 - n variables $\rightarrow 2^n$ minterms
 - E.g.: minterms for 3 variables

$x y z$	minterm	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0 0 0	$x'y'z'$ (m_0)	1	0	0	0	0	0	0	0
0 0 1	$x'y'z$ (m_1)	0	1	0	0	0	0	0	0
0 1 0	$x'y z'$ (m_2)	0	0	1	0	0	0	0	0
0 1 1	$x'yz$ (m_3)	0	0	0	1	0	0	0	0
1 0 0	$xy'z'$ (m_4)	0	0	0	0	1	0	0	0
1 0 1	$xy'z$ (m_5)	0	0	0	0	0	1	0	0
1 1 0	xyz' (m_6)	0	0	0	0	0	0	1	0
1 1 1	xyz (m_7)	0	0	0	0	0	0	0	1

■53

Maxterms

- **Maxterm**: standard sum, $M_j (= m_j')$
 - an **OR** term of the n variables, w/ each variable being **unprimed** if the corresponding bit is **0** and **primed** if a **1**.
 - n variables $\rightarrow 2^n$ Maxterms
 - E.g.: Maxterms for 3 variables

$x y z$	Maxterm	M_0	M_1	M_2	M_3	M_4	M_5	M_6	M_7
0 0 0	$x + y + z$ (M_0)	0	1	1	1	1	1	1	1
0 0 1	$x + y + z'$ (M_1)	1	0	1	1	1	1	1	1
0 1 0	$x + y' + z$ (M_2)	1	1	0	1	1	1	1	1
0 1 1	$x + y' + z'$ (M_3)	1	1	1	0	1	1	1	1
1 0 0	$x' + y + z$ (M_4)	1	1	1	1	0	1	1	1
1 0 1	$x' + y + z'$ (M_5)	1	1	1	1	1	0	1	1
1 1 0	$x' + y' + z$ (M_6)	1	1	1	1	1	1	0	1
1 1 1	$x' + y' + z'$ (M_7)	1	1	1	1	1	1	1	0

■54

minterms vs. Maxterms

- E.g.: for 3 binary variables ($* M_j = m_j'$)

$x y z$	minterm	Maxterm
000	$x'y'z'$ (m_0)	$x + y + z$ (M_0)
001	$x'y'z$ (m_1)	$x + y + z'$ (M_1)
010	$x'y z'$ (m_2)	$x + y' + z$ (M_2)
011	$x'yz$ (m_3)	$x + y' + z'$ (M_3)
100	$xy'z'$ (m_4)	$x' + y + z$ (M_4)
101	$xy'z$ (m_5)	$x' + y + z'$ (M_5)
110	xyz' (m_6)	$x' + y' + z$ (M_6)
111	xyz (m_7)	$x' + y' + z'$ (M_7)

– E.g.:

$$m_3 = \bar{x}yz \rightarrow \bar{m}_3 = \overline{\bar{x}yz} = x + \bar{y} + \bar{z} = M_3$$

J.J. Shann 2-55

■55

Canonical Forms

- Canonical forms:
 - A Boolean function can be expressed algebraically from a given **truth table** by
 - Sum-of-minterms form:**

$$(minterm) + \dots + (minterm)$$
 - form a **minterm** for each combination of the variables that produces a **1** in the function, and then take the **OR** of all those terms
 - Product-of-Maxterms form:**

$$(maxterm) \bullet \dots \bullet (maxterm)$$
 - form a **maxterm** for each combination of the variables that produces a **0** in the function, and then take the **AND** of all those terms

J.J. Shann 2-56

■56

Example

- Given the truth table of two functions, f_1 and f_2 , express each of the functions as sum-of-minterms and product-of-maxterms forms.

x	y	z	f_1	f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

<Ans.>

Sum of minterms:

$$f_1 = x'y'z + xy'z' + xyz = m_1 + m_4 + m_7 = \sum m(1, 4, 7)$$

$$f_2 = x'yz + xy'z + xyz' + xyz = m_3 + m_5 + m_6 + m_7 = \sum m(3, 5, 6, 7)$$

J.J. Shann 2-57

■57

x	y	z	f_1	f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$f_1 = x'y'z + xy'z' + xyz$$

$$= m_1 + m_4 + m_7 = \sum m(1, 4, 7)$$

$$f_2 = x'yz + xy'z + xyz' + xyz$$

$$= m_3 + m_5 + m_6 + m_7 = \sum m(3, 5, 6, 7)$$

Product of maxterms:

$$f_1' = m_0 + m_2 + m_3 + m_5 + m_6$$

$$= x'y'z' + x'yz' + x'yz + xy'z + xyz'$$

$$f_1 = (f_1')' = (x+y+z)(x+y'+z)(x+y'+z')(x'+y+z)(x'+y'+z)$$

$$= M_0 M_2 M_3 M_5 M_6 = \prod M(0, 2, 3, 5, 6)$$

$$f_2 = (x+y+z)(x+y+z')(x+y'+z)(x'+y+z)$$

$$= M_0 M_1 M_2 M_4 = \prod M(0, 1, 2, 4)$$

J.J. Shann 2-58

■58

Conversion to Sum of Minterms Form

- Two methods of expressing a Boolean function in its sum-of-minterms form:
 - Expand the expression into a **sum of AND terms** by using the distributive law, $x(y+z) = xy + xz$. Any missing variable x in each AND term is ANDed with $(x+x')$.
 - Obtain the **truth table** of the function directly from the algebraic expression and then read the **minterms** from the truth table.

J.J. Shann 2-59

■59

Example: $F(A, B, C) = A + B'C$

<Ans.>

Approach 1:

$$A = A(B+B')(C+C')$$

$$= (AB + AB')(C+C')$$

$$= AB(C+C') + AB'(C+C')$$

$$= ABC + ABC' + AB'C + AB'C'$$

$$B'C = (A+A')B'C$$

$$= AB'C + A'B'C$$

$$F(A, B, C) = A'B'C + AB'C' + AB'C + ABC' + ABC$$

$$= m_1 + m_4 + m_5 + m_6 + m_7$$

$$= \sum m(1, 4, 5, 6, 7)$$

J.J. Shann 2-60

■60

Approach 2:

$$F(A, B, C) = A + B'C$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned} F(A, B, C) &= A'B'C + AB'C' + AB'C \\ &\quad + ABC' + ABC \\ &= \Sigma m(1, 4, 5, 6, 7) \end{aligned}$$

J.J. Shann 2-61

61

Conversion to Product-of-Maxterms Form

Two methods of expressing a Boolean function in its product-of-maxterms form:

- Convert the function into **OR terms** by using the distributive law, $x + yz = (x + y)(x + z)$.
Any missing variable x in each OR term is ORed with xx' .
- Obtain the **truth table** of the function directly from the algebraic expression and then read the **maxterms** from the truth table.

J.J. Shann 2-62

62

Example: $F(x, y, z) = xy + x'z$

<Ans.>

Approach 1:

$$\begin{aligned} F &= xy + x'z \\ &= (xy + x')(xy + z) \\ &= (x+x')(y+x')(x+z)(y+z) \\ &= (x'+y)(x+z)(y+z) \end{aligned}$$

$$\begin{aligned} x'+y &= x' + y + zz' \\ &= (x'+y+z)(x'+y+z') \end{aligned}$$

$$\begin{aligned} x+z &= x + z + yy' \\ &= (x+y'+z)(x+y'+z) \end{aligned}$$

$$\begin{aligned} y+z &= y + z + xx' \\ &= (x+y'+z)(x'+y+z) \end{aligned}$$

$$\begin{aligned} F &= (x'+y+z)(x+y'+z)(x'+y+z)(x'+y+z') \\ &= M_0 M_2 M_4 M_5 \\ &= \Pi M(0, 2, 4, 5) \end{aligned}$$

J.J. Shann 2-63

63

Approach 2:

$$F(x, y, z) = xy + x'z$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned} F(x, y, z) &= (x+y+z)(x+y'+z) \\ &\quad (x'+y+z)(x'+y+z') \\ &= \Pi M(0, 2, 4, 5) \end{aligned}$$

J.J. Shann 2-64

64

Conversion b/t Canonical Forms

■ To convert from one canonical form to another:

- Interchange the symbols Σ and Π & list those numbers missing from the original form
- E.g.: $F = xy + x'z$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



$$\begin{aligned}
 F(x, y, z) &= \Sigma m(1, 3, 6, 7) \\
 &= \dots\dots \\
 &= \Pi M(0, 2, 4, 5) \\
 &= \dots\dots
 \end{aligned}$$

J.J. Shann 2-65

■65

B. Standard Forms

■ Canonical forms: special cases of standard forms

- sum of *minterms* & product of *maxterms*
- the basic forms that one obtains from reading a function from the *truth table*.
- Each terms must contain *all* the variables
 - Seldom w/ the least # of literals (not minimized)

■ Standard forms:

- Sum of *products* & product of *sums*
 (*AND terms*) (*OR terms*)
- The terms may contain *any* number of literals

J.J. Shann 2-66


■66

Sum of Products (SOP)

■ SOP: $(AND\ term) + \dots + (AND\ term)$

- is a Boolean expression containing *AND terms* (*product terms*) of one or more literals each.
- There *AND terms* are *ORing* together.
- → *2-level gating structure*
 (if the complements of the input variables are available)

- E.g.: $F_1 = y' + xy + x'yz'$

 

J.J. Shann 2-67


■67

Product of Sums (POS)

■ POS: $(OR\ term) \cdot \dots \cdot (OR\ term)$

- is a Boolean expression containing *OR terms* (*sum terms*) of one or more literals each.
- These *OR terms* are *ANDing* together.
- → *2-level gating structure*
 (if the complements of the input variables are available)

- E.g.: $F_2 = x(y'+z)(x'+y+z')$

 

J.J. Shann 2-68

■68

C. Nonstandard Form

■ Nonstandard form:


– E.g.: $F = AB + C(D + E)$ → 3-level

■ Nonstandard form → Standard form:

– By using the distributive laws

– E.g.: $F = AB + C(D + E)$
 $= AB + CD + CE$ → 2-level

Standard form
vs
Nonstandard
form

 

■69

2-7

Other Logic Operations

J.J. Shann

■70

Other Logic Operations

■ Basic logic operations: AND, OR, NOT

■ All possible functions of n binary variables:

n binary variables → 2^n distinct minterms

→ 2^{2^n} possible functions

■ E.g.: $n = 2$ → 4 minterms → 16 possible functions

	x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
m_0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
m_1	0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
m_2	1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
m_3	1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

J.J. Shann 2-71

■71

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

$F_0 = 0$	Null	$F_{15} = 1$	Identity
$F_1 = xy$	AND, $x \cdot y$	$F_{14} = (xy)'$	NAND, $x \uparrow y$
$F_2 = xy'$	Inhibition, x/y	$F_{13} = x' + y$	Implication, $x \supset y$
$F_3 = x$	Transfer	$F_{12} = x'$	Complement, x'
$F_4 = x'y$	Inhibition, y/x	$F_{11} = x + y'$	Implication, $x \subset y$
$F_5 = y$	Transfer	$F_{10} = y'$	Complement, y'
$F_6 = xy' + x'y$	Exclusive-OR, $x \oplus y$	$F_9 = xy + x'y'$	Equivalence, $(x \oplus y)'$
$F_7 = x + y$	OR, $x + y$	$F_8 = (x + y)'$	NOR, $x \downarrow y$

J.J. Shann 2-72

■72

$F_0 = 0$	Null	$F_{15} = 1$	Identity
$F_1 = xy$	AND, $x \cdot y$	$F_{14} = (xy)'$	NAND, $x \uparrow y$
$F_2 = xy'$	Inhibition, x/y	$F_{13} = x' + y$	Implication, $x \supset y$
$F_3 = x$	Transfer	$F_{12} = x'$	Complement, x'
$F_4 = x'y$	Inhibition, y/x	$F_{11} = x + y'$	Implication, $x \subset y$
$F_5 = y$	Transfer	$F_{10} = y'$	Complement, y'
$F_6 = xy' + x'y$	Exclusive-OR, $x \oplus y$	$F_9 = xy + x'y'$	Equivalence, $(x \oplus y)'$
$F_7 = x + y$	OR, $x + y$	$F_8 = (x + y)'$	NOR, $x \downarrow y$

— The 16 functions can be subdivided into 3 categories:

1. 2 functions that produce a **constant 0** or **1**.
2. 4 functions w/ **unary** operations **complement (NOT)** and **transfer**.
3. 10 functions w/ **binary** operators that define eight different operations **AND**, **OR**, **NAND**, **NOR**, **exclusive-OR**, **equivalence**, **inhibition**, and **implication**.

J.J. Shann 2-73

■73

2-8

Digital Logic Gates

J.J. Shann

■74

Digital Logic Gates

- **Boolean expression:**
 - **AND**, **OR** and **NOT** operations
 - It is easier to implement a Boolean function in these types of gates.
- **Factors in considering the construction of other types of logic gates:**
 - the **feasibility** and **economy** of implementing the gate w/ electronic components
 - the possibility of **extending** the gate to more than two inputs
 - the basic **properties** of the binary operator

* **Why?** > E.g.: **commutativity**, **associativity**, ...

* **Why?** — the ability of the gate to implement Boolean functions alone or in conjunction w/ other gates

J.J. Shann 2-75

■75

$F_0 = 0$	Null	$F_{15} = 1$	Identity
$F_1 = xy$	AND, $x \cdot y$	$F_{14} = (xy)'$	NAND, $x \uparrow y$
$F_2 = xy'$	Inhibition, x/y	$F_{13} = x' + y$	Implication, $x \supset y$
$F_3 = x$	Transfer	$F_{12} = x'$	Complement, x'
$F_4 = x'y$	Inhibition, y/x	$F_{11} = x + y'$	Implication, $x \subset y$
$F_5 = y$	Transfer	$F_{10} = y'$	Complement, y'
$F_6 = xy' + x'y$	Exclusive-OR, $x \oplus y$	$F_9 = xy + x'y'$	Equivalence, $(x \oplus y)'$
$F_7 = x + y$	OR, $x + y$	$F_8 = (x + y)'$	NOR, $x \downarrow y$

- **Consider the 16 functions:**
 - two are equal to a constant **0, 1**
 - four are repeated twice **Transfer, Complement, Inhibition, Implication**
 - **inhibition** and **implication** are **not** commutative or associative (\times)
 - **complement, transfer, AND, OR, NAND, NOR, XOR**, and **equivalence (XNOR)** are used as standard gates
 - > complement: inverter, NOT
 - > transfer: buffer (drive strength)


* **NAND and NOR gates are far more popular than the AND and OR gates.**

J.J. Shann 2-76

■76

AND, OR


AND

 

$$F = xy$$

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

OR

 

$$F = x + y$$


x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

J.J. Shann 2-77

■77

Inverter, Buffer


Inverter

 

$$F = x'$$

x	F
0	1
1	0

Buffer

 

$$F = x$$


x	F
0	0
1	1

J.J. Shann 2-78

■78

NAND, NOR


NAND

 

$$F = (xy)'$$

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 

$$F = (x + y)'$$


x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

J.J. Shann 2-79

■79

XOR, NXOR

XOR

 


$$F = xy' + x'y$$

$$= x \oplus y$$

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

 

$$F = xy + x'y'$$

$$= (x \oplus y)'$$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

J.J. Shann 2-80

■80

Extension to Multiple Inputs

■ Extension to multiple inputs

- A gate can be extended to multiple inputs if its binary operation is **commutative** and **associative**.

■ AND, OR: commutative and associative:

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x \cdot y = y \cdot x$$

$$(x \cdot y) \cdot z = x \cdot (y \cdot z)$$

J.J. Shann 2-81

■81


■ NAND (\uparrow), NOR (\downarrow):

- commutative but **not** associative \Rightarrow not extendable

- E.g.: $(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$


$$(x \downarrow y) \downarrow z = [(x + y)' + z]' = (x + y) z' = xz' + yz'$$
 
$$x \downarrow (y \downarrow z) = [x + (y + z)']' = x' (y + z) = x'y + x'z$$



$$(x \downarrow y) \downarrow z = (x + y)z'$$

$$\Sigma m(2, 4, 6)$$

 

$$x \downarrow (y \downarrow z) = x'(y + z)$$

$$\Sigma m(1, 2, 3)$$

J.J. Shann 2-82


■82

- Modification of the definition:


- The multiple NOR (or NAND) gate is a **complement OR** (or **AND**) gate.

$$x \downarrow y \downarrow z = (x + y + z)'$$
 
$$x \uparrow y \uparrow z = (x \cdot y \cdot z)'$$



3-input NOR gate

 

3-input NAND gate


J.J. Shann 2-83

■83


- In writing cascaded NOR and NAND operations:

- Use the correct **parentheses** to signify the proper sequence of the gates.

- E.g.: Cascaded NAND gates

 

$$F = [(ABC)' \cdot (DE)']' = ABC + DE$$

 


$$G = (ABCDE)' = A' + B' + C' + D' + E'$$

J.J. Shann 2-84

■84


■ Exclusive-OR (\oplus) and Equivalence:

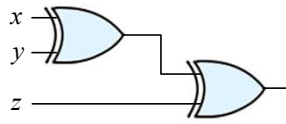- are commutative and associative
- Modification of the definition of multiple-input XOR:
 - an **odd function**: = 1, if the input variables have an odd # of 1's



x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Using 2-input gates

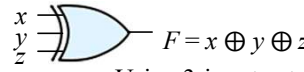

Using 3-input gate

- Equivalence: an **even function**

■85

Positive & Negative Logic

■ Logic-value assignment: polarity assignment

- Positive logic
- Negative logic

Signal value

Logic value

H 1

L 0

Positive logic

Signal value

Logic value

H 0

L 1

Negative logic

J.J. Shann 2-86

■86

■ Demonstration of positive & negative logic:

x	y	z
L	L	L
L	H	L
H	L	L
H	H	H

H = 1
L = 0

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1


H = 0
L = 1

x	y	z
1	1	1
1	0	1
0	1	1
0	0	0


Truth table with H and L

Truth table for positive logic


Truth table for negative logic

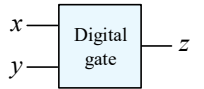

Gate block diagram

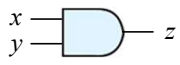

Positive logic AND gate

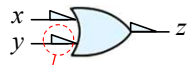

Negative logic OR gate

* Polarity indicator 2-87

■87

■ Conversion b/t positive and negative logic:

- Change 1's to 0's and 0's to 1's in both inputs and output of a gate (truth table)
 - ⇒ take the **dual** of a function
 - (AND → OR, OR → AND, 0 → 1, 1 → 0)

* Duality principle

J.J. Shann 2-88

■88

2-9



Integrated Circuits (ICs)

J.J. Shann

■89

Integrated Circuits (ICs)

  - Digital ckt's are constructed w/ integrated ckt's.
- Integrated circuit (IC):
 - is a silicon semiconductor crystal (chip) containing the electronic components for the **digital gates** and **storage elements**.
 - The various components are interconnected on the chip.
 - The chip is mounted in a ceramic or plastic container, and connections are welded from the chip to the external pins.



J.J. Shann 2-90

■90

A. Levels of Integration

- Levels of integration: ckt complexity
(# of logic gates in a single silicon chip)
 - **SSI**: small-scale integration, <10 gates
 - **MSI**: medium-scale integration, 10 ~ 100 (Ch 4~7)
 - performs specific elementary digital functions
 - e.g.: addition of 4 bits
 - **LSI**: large-scale integration: 100 ~ x000
 - eg.: small processors, small memories, programmable modules
 - **VLSI**: very large-scale integration, x000 ~
 - e.g.: complex microprocessors, digital signal processing chips

J.J. Shann 2-91

■91

B. Digital Logic Families

- Digital logic families: ckt technology

TTL:	transistor-transistor logic
ECL:	emitter-coupled logic (speed)
MOS:	metal-oxide semiconductor (density)
CMOS:	complementary MOS (power)

 - The basic ckt in each family is a **NAND**, **NOR**, or **inverter** gate. (Ch3)

J.J. Shann 2-92

■92

(Supplementary materials)

補充資料：Technology Parameters

- The most important parameters of digital logic families:
 - Fan-in
 - Fan-out
 - Noise margin
 - Propagation delay
 - Cost
 - Power dissipation

Reference:


M. Morris Mano & Charles R. Kime, *Logic and Computer Design Fundamentals*, 3rd Edition, 2004, Pearson Prentice Hall. (§3-2)

J.J. Shann 2-93

■93

Fan-in

 - **Fan-in**: # of inputs available on a gate
 - For high-speed technologies, fan-in is often restricted on gate primitives to ≤ 4 or 5.
- E.g.: Implementation of a 7-input NAND gate using NAND gates w/ 4 or fewer inputs



* NAND is not associative!

J.J. Shann 2-96

■96

Fan-Out

- **Fan-out**: # of standard loads driven by a gate output
 - *Max fan-out*: the fan-out that the output can drive w/o impairing gate performance
- For CMOS gates:
 - The load on the output of a gate determines the time required for the output of the gate to change from L to H and from H to L. → *transition time*


J.J. Shann 2-97

■97

Example:

An integrated circuit logic family has NAND gates with a fan-out of 4 standard loads & buffers with a fan-out of 8 standard loads. Sketch a schematic showing how the output signal of a single NAND gate can be applied to 18 other gate inputs. Assume that each input is one standard load.

<Ans.>

 

J.J. Shann 2-98

■98

★

- **Fan-in & Fan-out:**
 - must be dealt w/ in the **technology mapping step** of the design process.
 - Gate w/ fan-ins larger than available \Rightarrow Multiple gates
 - Gate w/ fan-outs either exceed its max allowable fan-out or have too high a delay \Rightarrow Multiple gates or added buffers at its output

J.J. Shann 2-99

■99

Noise Margin

- **Noise margin:** the max external noise voltage superimposed on a normal input value that will not cause an undesirable change in the ckt output

(p.1-8)

J.J. Shann 2-100

■100

Propagation Delay

- **Propagation delay:** the time required for a change in value of a signal to propagate from input to output
 - The operating speed of a ckt is inversely related to the **longest propagation delays** through the gates of the ckt.
- 3 propagation delay parameters:
 - high-to-low propagation time t_{PHL}
 - low-to-high propagation time t_{PLH}
 - propagation delay $t_{pd} : \max(t_{PHL}, t_{PLH})$

J.J. Shann 2-101


■101

- 3 propagation delay parameters:
 - high-to-low propagation time t_{PHL}
 - low-to-high propagation time t_{PLH}
 - propagation delay $t_{pd} : \max(t_{PHL}, t_{PLH})$
- E.g.:

$t_{pd} = \max(t_{PHL}, t_{PLH})$

J.J. Shann 2-102

■102

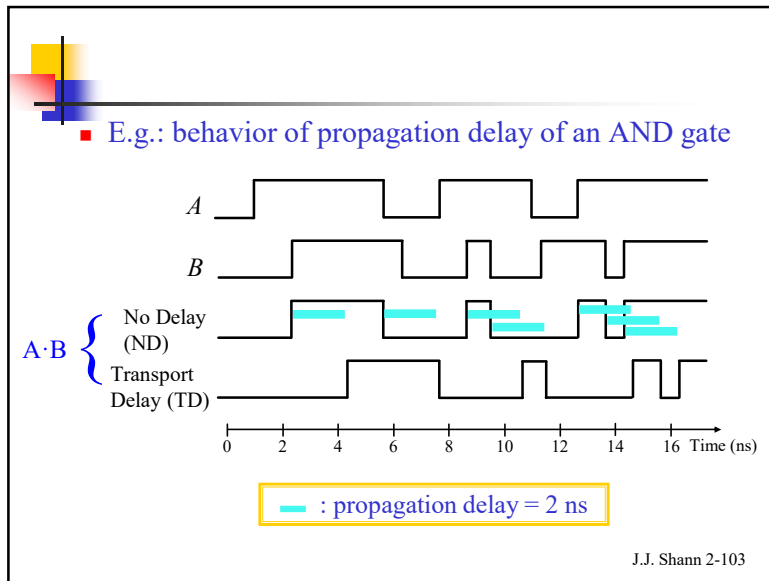

■103

- For CMOS gates:
- The load on the output of a gate determines the time required for the output of the gate to change from L to H and from H to L. → *transition time*
- E.g.: (next page)
- J.J. Shann 2-104

■104

■ E.g.: Calculation of gate delay based on fan-out

A 4-input NAND gate output is attached to the inputs of the following gates w/ the given # of standard loads representing their inputs:

- 4-input NOR gate-- 0.80 standard load
- 3-input NAND gate-- 1.00 standard load
- Inverter-- 1.00 standard load

The formula for the delay of the 4-input NAND gate is

$$t_{pd} = 0.07 + 0.021 \times SL \text{ ns}$$

SL: the sum of the standard loads driven by the gate

<Ans.> Ignoring the wiring delay

$$t_{pd} = 0.07 + 0.021 \times (0.80 + 1.00 + 1.00) = 0.129 \text{ ns}$$

J.J. Shann 2-105

■105

- Cost**
- **Cost** for a gate:
- is usually based on the **area** occupied by the layout cell (\propto the size of the transistors & the wiring in the gate layout)
- J.J. Shann 2-106

■106

Power dissipation

- **Power dissipation:** the power drawn from the power supply and consumed by the gate
 - must be considered in relation to the **operating temperature** and **cooling**

J.J. Shann 2-107

■107

C. Computer-Aided Design (CAD) of VLSI Circuits

- CAD tools:
 - software programs that support computer-based representation and aid in the development of digital hardware by automating the design process.
 - Schematic capture tools:
 - support the drawing of blocks and interconnections at all levels of the hierarchy.
 - At the level of **primitives** and **functional blocks**, libraries of graphics symbols are provided.
 - Logic simulator:
 - verify the **behavior** and the **timing** of the hierarchical blocks and the entire ckt
 - Logic synthesizer:
 - optimize design being generated automatically from HDL (hardware description language) specifications in physical **area** or **delay**

J.J. Shann 2-108

■108

* Chapter Summary

- Primitive logic ops: AND, OR, NOT
- Boolean algebra
- Canonical form: minterm & maxterm standard forms
- Standard forms: SoP and PoS \Rightarrow 2-level gate ckt
- Other logic gates:
 - NAND, NOR
 - XOR, XNOR
- Integrated circuits
 - Technology parameters

J.J. Shann 2-109

■109