


# Chapter 3

---


## Gate-Level Minimization

*J.J. Shann*

1



### Contents


- 3-1 Introduction
  - 補充資料：Cost Criteria
- 3-2 The Map Method
- 3-3 Four-Variable Map
- 補充資料：Five-Variable Map
- 3-4 **Product-of-Sums (PoS)** Simplification
- 3-5 Don't-Care Conditions
- 補充資料：Quine-McCluskey Method (Tabular Method) 
- 補充資料：Multiple-Level Circuit Optimization

---

- 3-6 NAND and NOR Implementation
- 3-7 Other Two-Level Implementations
- 3-8 Exclusive-OR Function
- 3-9 Hardware Description Language (HDL)

J.J. Shann 3-2

2

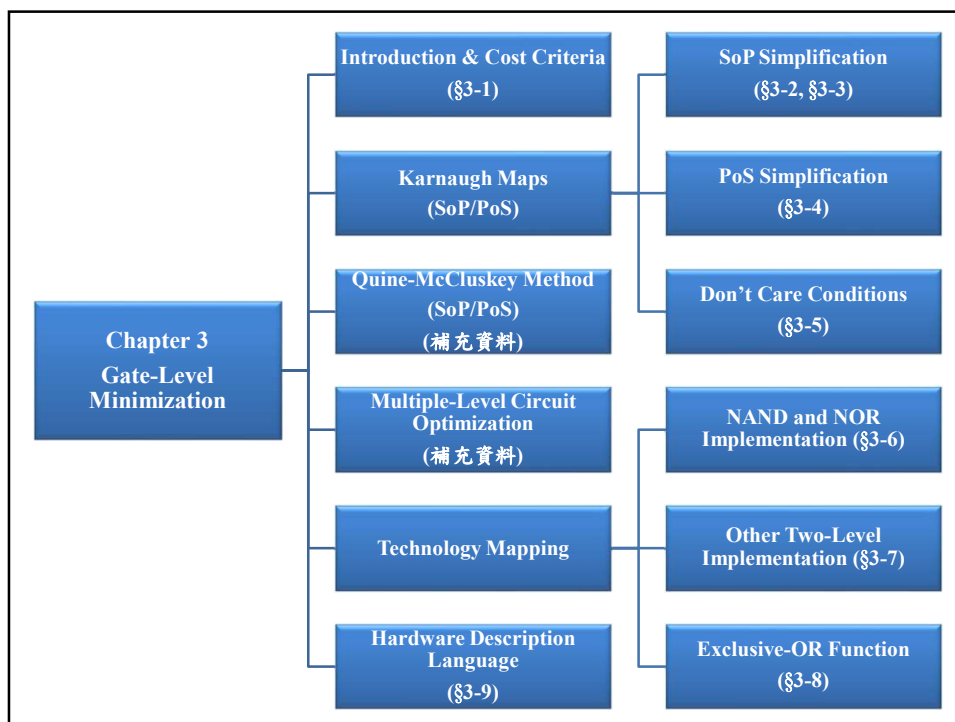


3

## Exercises in Textbook (6<sup>th</sup> ed)

Sections	Exercises	Typical Ones
§3-2	3.1~3.3	3.3(a)*
§3-3	3.4~3.12, 3.26	3.5(b)*, 3.6(b)*, 3.10(b)
§3-4	3.13, 3.14	3.13(b)
§3-5	3.15	3.15(b)*
補充資料 Tabular Method		Repeat 3-15(b) by Quine-McCluskey method
§3-6	3.16~3.23	3.16(a), 3.20
§3-7	3.24, 3.25	3.24
§3-8	3.27, 3.28, 3.30	3.28
Ch4	3.29	
HDL	3.31~3.40	

\* : Answers to problems appear at the end of the text. J.J. Shann 3-4

4




# 3-1

---

## Introduction

J.J. Shann

5



## Introduction

- Representation of a Boolean function:
  - Truth table: unique
  - Algebraic expression: many different forms  
⇒ digital logic circuit
- Minimization of Boolean function:
  - Algebraic manipulation: literal minimization (§2-5)
    - use the rules and laws of *Boolean algebra*
    - Disadv.: It lacks specific rules to predict each succeeding step in the manipulation process.
  - ↪ – Map method: gate-level minimization (Ch3)
    - gate-level ➢ simple straightforward procedure ⇒ Manual design of simple ckts
    - minimization ➢ Disadv.: Maps for more than 4 variables are not simple to use.
  - ↪ – Tabular method: Quine-McCluskey method (補充資料)
    - systematic procedure ⇒ Computer-based logic synthesis tools

J.J. Shann 3-6

6

(Supplementary materials)

## 補充資料：Cost Criteria

### ■ Two cost criteria:

- i. Literal cost
  - the # of literal appearances in a Boolean expression
- ii. Gate input cost (✓)
  - the # of inputs to the gates in the implementation

### Reference:

M. Morris Mano & Charles R. Kime, *Logic and Computer Design Fundamentals*, 3<sup>rd</sup> Edition, 2004, Pearson Prentice Hall.  
(§2-4)

J.J. Shann 3-7

7

## Literal Cost

### ■ Literal cost:

- the # of literal appearances in a Boolean expression
- E.g.:  $F = AB + C(D + E) \rightarrow 5$  literals (p.2-69)  
 $F = AB + CD + CE \rightarrow 6$  literals
- Adv.: is very simple to evaluate by counting literal appearances
- Disadv.: does not represent ckt complexity accurately in all cases
  - E.g.:

$$G = ABCD + \overline{A}\overline{B}\overline{C}\overline{D} \rightarrow 8 \text{ literals}$$

$$G = (\overline{A} + B)(\overline{B} + C)(\overline{C} + D)(\overline{D} + A) \rightarrow 8 \text{ literals}$$

J.J. Shann 3-8

8

## Gate Input Cost

### ■ Gate input cost (GIC):

- the # of inputs to the gates in the implementation
- is a good measure for contemporary logic implementation
  - is proportional to the # of transistors and wires used in implementing a logic ckt. (especially for ckt  $\geq 2$  levels)


J.J. Shann 3-9

9
 
### ■ E.g.: nonstandard vs. standard form (p.2-69)


$$F = AB + C(D + E) \rightarrow 3\text{-level (5 literals)}$$

$$= AB + CD + DE \rightarrow 2\text{-level (6 literals)}$$



$$AB + C(D + E)$$

**GIC = 8**

 


$$AB + CD + CE$$

**GIC = 9**


J.J. Shann 3-10

10




■ E.g.:  $G = ABCD + \overline{A}\overline{B}\overline{C}\overline{D}$  → GIC = ?

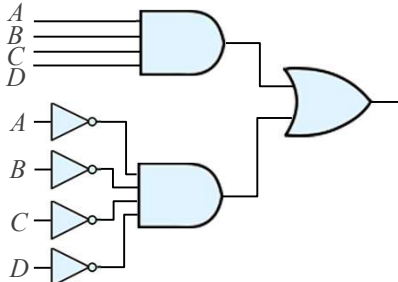$G = (\overline{A} + B)(\overline{B} + C)(\overline{C} + D)(\overline{D} + A)$  → GIC = ?




**GIC = 4 + 2 × 4 + 2 = 14**

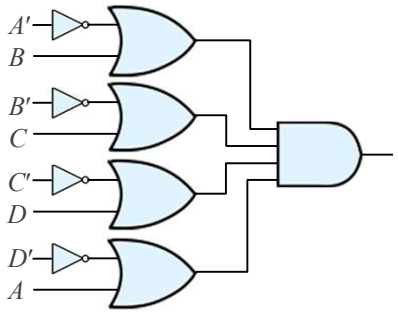

**GIC = 4 + 4 × 2 + 4 = 16**

J.J. Shann 3-11

11



■ For SoP or PoS eqs, GIC = the sum of

- all literal appearances
- the # of terms excluding terms that consist only of a single literal
- the # of distinct complemented single literals (optional)
- E.g.: p.3-10

$G = ABCD + \overline{A}\overline{B}\overline{C}\overline{D}$  → GIC = 8 + 2 (+ 4)

$G = (\overline{A} + B)(\overline{B} + C)(\overline{C} + D)(\overline{D} + A)$  → GIC = 8 + 4 (+ 4)

J.J. Shann 3-12

12



3-2

## The Map Method

J.J. Shann

13



## The Map Method

$$XY + XY' = X$$

- Map method: Karnaugh map simplification
  - a simple straightforward procedure
  - **K-map**: a pictorial form of a truth table
    - a diagram made up of squares  **$n$  input variables  $\rightarrow 2^n$  squares**
    - Each square represents one **minterm** of the function.
    - **Any adjacent squares in the map differ by only one variable.**
  - The simplified expressions produced by the map are always in one of the two **standard forms**:
    - **SOP** (sum of products) or **POS** (product of sums)
- The simplest algebraic expression: not unique
  - one w/ a minimum **# of terms** and  
w/ the fewest possible **# of literals per term**.
  - ⇒ a ckt diagram w/ a minimum **# of gates** and  
the minimum **# of inputs to the gate**.

J.J. Shann 3-14

14

## A. Two-Variable Map

- Two-variable map: 2 variables  $\rightarrow$  4 minterms
  - 4 squares, one for each minterm.
  - A function of 2 variables can be represented in the map by marking the squares that correspond to the **minterms** of the function.

$F(X,Y)$

	$Y$	0	1
$X$	0	$X'Y'$	$X'Y$
	1	$XY'$	$XY$

	$X$	0	1
$Y$	0	$X'Y'$	$XY'$
	1	$X'Y$	$XY$

\* Any adjacent squares in the map differ by only one variable.

$\Rightarrow$  2 adjacent minterms may be combined into a term with 1 literal removed.

$$(xy + xy' = x)$$

J.J. Shann 3-15

15

## Example: 2-Variable K-Map

■  $F(X,Y) = m_1 + m_2 + m_3$

	$Y$	0	1
$X$	0		1
	1	1	1

$\Rightarrow F = X + Y$

$$\begin{aligned}
 F_2 &= m_1 + m_2 + m_3 \\
 &= \overline{X}Y + X\overline{Y} + XY \\
 &= \overline{X}Y + X(\overline{Y} + Y) \\
 &= \overline{X}Y + X \\
 &= (\overline{X} + X)(Y + X) \\
 &= X + Y
 \end{aligned}$$

by applying Boolean algebra

	$Y$	0	1
$X$	0	$X'Y'$	$X'Y$
	1	$XY'$	$XY$

by combining squares in the map

J.J. Shann 3-16

16



## B. Three-Variable Map

- Three-variable map: 8 minterms  $\Rightarrow$  8 squares

$F(X,Y,Z)$

x \ yz	00	01	11	10
	0	1	3	2
0	$X'Y'Z'$	$X'Y'Z$	$X'YZ$	$X'YZ'$
1	$XY'Z'$	$XY'Z$	$XYZ$	$XYZ'$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

- Only one bit changes in value from one adjacent column to the next
  - Any two adjacent squares in the map differ by only one variable, which is primed in one square and unprimed in the other.
  - E.g.:  $m_5$  &  $m_7$
- Note: Each square has 3 adjacent squares.
  - The right & left edges touch each other to form adjacent squares.
  - E.g.:  $m_4 \rightarrow m_0, m_5, m_6$

J.J. Shann 3-17

17

- Alternatives of 3-variable map:

x \ yz	00	01	11	10
	0	1	3	2
0	$X'Y'Z'$	$X'Y'Z$	$X'YZ$	$X'YZ'$
1	$XY'Z'$	$XY'Z$	$XYZ$	$XYZ'$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

z \ xy	00	01	11	10
	0	2	6	4
0	$X'Y'Z'$	$X'YZ'$	$XY'Z'$	$XYZ'$
1	$X'Y'Z$	$X'YZ$	$XY'Z$	$XYZ$

$m_0$	$m_2$	$m_6$	$m_4$
$m_1$	$m_3$	$m_7$	$m_5$

J.J. Shann 3-18

18

## ■ Alternatives of 3-variable map: (cont'd)

$F(X,Y,Z)$

		<b>Z</b>	0	1
<b>XY</b>	00		0	1
	01		2	3
	11		6	7
	10		4	5

		<b>X</b>	0	1
<b>YZ</b>	00		0	4
	01		1	5
	11		3	7
	10		2	6

J.J. Shann 3-19

19

## Map Minimization of SOP Expression

### ■ Basic property of adjacent squares:

		<b>YZ</b>	00	01	11	10
<b>X</b>	0		0 $X'Y'Z'$	1 $X'Y'Z$	3 $X'YZ$	2 $X'YZ'$
	1		4 $XY'Z'$	5 $XY'Z$	7 $XYZ$	6 $XYZ'$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

- Any two adjacent squares in the map differ by only one variable: primed in one square and unprimed in the other
  - E.g.:  $m_5 = X\bar{Y}Z$ ,  $m_7 = XYZ$

⇒ Any two minterms in adjacent squares that are ORed together can be simplified to a single AND term w/ a removal of the different variable.

- E.g.:  $m_5 + m_7 = X\bar{Y}Z + XYZ = XZ(\bar{Y} + Y) = XZ$

J.J. Shann 3-20

20

■ Procedure of map minimization of SOP expression:

i. A 1 is marked in each minterm that represents the function.

➤ Two ways:

(1) Convert each minterm to a binary number and then mark a 1 in the corresponding square.

(2) Obtain the coincidence of the variables in each term.

ii. Find possible adjacent  $2^k$  squares:

➤ 2 adjacent squares (i.e., minterms) → remove 1 literal

➤ 4 adjacent squares (i.e., minterms) → remove 2 literal

➤  $2^k$  adjacent squares (i.e., minterms) → remove  $k$  literal

⇒ The larger the # of squares combined, the less the # of literals in the product (AND) term.

\* It is possible to use the same square more than once.

J.J. Shann 3-21

21

■ Example 3.1

■ Simplify the Boolean function

$$F(X, Y, Z) = \sum m(2, 3, 4, 5)$$

<Ans.>

		Y			
		YZ			
X	YZ	00	01	11	10
		0	1	3	2
0		0	1	1	1
1		1	1		
				7	6

Annotations: A red dashed box groups minterms 2, 3, 6, 7 (YZ=10), labeled  $\overline{X}Y$ . A blue dashed box groups minterms 4, 5 (YZ=01), labeled  $X\overline{Y}$ .

$$F = \overline{X}Y + X\overline{Y}$$


J.J. Shann 3-22

22
 
## Example: 4-minterm Product Terms

- Product terms using 4 minterms
- $F(X, Y, Z) = \Sigma m(0, 2, 4, 6)$

\* The right & left edges touch each other to form adjacent squares.




$$\begin{aligned}
 m_0 + m_2 + m_4 + m_6 &= \overline{X}\overline{Y}\overline{Z} + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} + XY\overline{Z} \\
 &= \overline{X}\overline{Z}(\overline{Y} + Y) + X\overline{Z}(\overline{Y} + Y) \\
 &= \overline{X}\overline{Z} + X\overline{Z} = \overline{Z}(\overline{X} + X) = \overline{Z}
 \end{aligned}$$

J.J. Shann 3-23

23
 
## Example: 4-minterm Product Terms

- $F(X, Y, Z) = \Sigma m(0, 1, 2, 3, 6, 7)$



$$F = \overline{X} + Y$$

\* It is possible to use the same square more than once.

J.J. Shann 3-24

24

### Example 3.2: Redundant Terms

- Simplify the Boolean function

$$F(X,Y,Z) = \sum m(3,4,6,7)$$

<Ans.>

		Y			
		YZ		11	10
X	0	0	1	1	2
	1	1	5	1	1

*XY* → redundant (×)

$$F(X,Y,Z) = YZ + X\bar{Z}$$

J.J. Shann 3-25

25

### Example 3.3

- Simplify the Boolean function

$$F(X,Y,Z) = \sum m(0,2,4,5,6)$$

<Ans.>

		Y			
		YZ		11	10
X	0	1	1	3	2
	1	1	1	7	6

$$F(X,Y,Z) = \bar{Z} + X\bar{Y}$$

J.J. Shann 3-26

26

## Non-unique Optimized Expressions

- There may be alternative ways of combining squares to product equally optimized expressions:

E.g.:  $F(X,Y,Z) = \sum m(1,3,4,5,6)$

		Y			
		YZ			
X		00	01	11	10
	0	0	1	1	2
	1	1	1	7	6
		Z			

$$\begin{aligned}
 F(X,Y,Z) &= \sum m(1,3,4,5,6) \\
 &= \bar{X}Z + X\bar{Z} + \bar{X}\bar{Y} \\
 &= \bar{X}Z + X\bar{Z} + \bar{Y}Z
 \end{aligned}$$

J.J. Shann 3-27

27

## Simplifying Functions not Expressed as Sum-of-minterms Form

- If a function is not expressed as a sum of minterms:
  - use the map to obtain the minterms of the function & then simplify the function

- Example 3.4: Given the Boolean function

$$F = A'C + A'B + AB'C + BC$$

<Ans.>

$$F = A'C + A'B + AB'C + BC$$

$$\begin{aligned}
 &0-1 \quad 01- \quad 101 \quad -11 \\
 &1, 3 \quad 2, 3 \quad 5 \quad 3, 7
 \end{aligned}$$


$$= \sum m(1, 2, 3, 5, 7)$$

$$= C + A'B$$

		BC			
		00	01	11	10
A	0	0	1	1	2
	1	4	5	1	6

J.J. Shann 3-28

28




# 3-3

## Four-Variable Map

*J.J. Shann*

29



# Four-Variable Map

- Four-variable map: 16 minterms  $\Rightarrow$  16 squares

YZ

WX

00

01

11

10

00

01

11

10

0

1

3

2

4

5

7

6

12

13

15

14

8

9

11

10

$F(W, X, Y, Z)$

00

01

11

10

$m_0$

$m_1$

$m_3$

$m_2$

$m_4$

$m_5$

$m_7$

$m_6$

$m_{12}$

$m_{13}$

$m_{15}$

$m_{14}$

$m_8$

$m_9$

$m_{11}$

$m_{10}$

— Note: Each square has 4 adjacent squares.

- The map is considered to lie on a surface w/ the top and bottom edges, as well as the right and left edges, touching each other to form adjacent squares.
- E.g.:  $m_8 \rightarrow m_0, m_9, m_{10}, m_{12}$

J.J. Shann 3-30

30

- Alternatives of 4-variable map:

$$F(W,X,Y,Z)$$

YZ \ WX	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

WX \ YZ	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

J.J. Shann 3-31

31

### Example 3.5

- Simplify the Boolean function

$$F(W, X, Y, Z) = \Sigma(0,1,2,4,5,6,8,9,12,13,14)$$

<Ans.>

YZ \ WX	00	01	11	10
00	1	1		1
01	1	1		1
11	1	1		1
10	1	1		

$$F = \bar{Y} + WZ + XZ$$

J.J. Shann 3-32

32



### Example 3.6

- Simplify the Boolean function

$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

<Ans.>

		CD			
		00	01	11	10
AB	00	1 <sub>0</sub>	1 <sub>1</sub>		1 <sub>2</sub>
	01				1 <sub>6</sub>
	11				
	10	1 <sub>8</sub>	1 <sub>9</sub>		1 <sub>10</sub>

$$F = B'D' + B'C' + A'CD'$$

J.J. Shann 3-33

33

### Map Manipulation

- When choosing adjacent squares in a map:
  - Ensure that **all the minterms** of the function are covered when combining the squares.
  - Minimize the # of **terms** in the expression.
    - avoid any **redundant terms** whose minterms are already covered by other terms

J.J. Shann 3-34

34

## Prime Implicants

### ■ *Implicant:*

- A **product term** is an implicant of a function if the function has the value 1 for all minterms of the product term.

### ■ *Prime implicant: PI*

- a product term obtained by combining the max. possible # of adjacent squares in the map

### ■ *Essential prime implicant: EPI, must be included*

- If a minterm in a square is covered by only one PI, that PI is said to be essential.
  - Look at each square marked w/ a 1 and check the # of PIs that cover it.

J.J. Shann 3-35

35

## Example

### ■ Find the PIs and EPIs of the Boolean function

$$F(X, Y, Z) = \sum m(1, 3, 4, 5, 6)$$

<Ans.>

		Y			
	YZ	00	01	11	10
X	0	0	1	1*	2
	1	1	1		1*
		Z			

4 PIs:  $\bar{X}Z$ ,  $\bar{Y}Z$ ,  $X\bar{Z}$ ,  $X\bar{Y}$

2 EPIs:  $\bar{X}Z$  ( $m_3$ ),  $X\bar{Z}$  ( $m_6$ )

$$\begin{aligned}
 F(X, Y, Z) &= \sum m(1, 3, 4, 5, 6) \\
 &= \bar{X}Z + X\bar{Z} + X\bar{Y} \\
 &= \bar{X}Z + X\bar{Z} + \bar{Y}Z
 \end{aligned}$$


J.J. Shann 3-36

36

## Example

- Find the PIs and EPIs of the Boolean function  
 $F(A,B,C,D) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$

<Ans.>

 


PIs: EPIs:  
 CD  $B'D' (m_0)$   
 BD  $BD (m_5)$   
 AD  
 AB'  
 B'C  
 B'D'

J.J. Shann 3-37


37

## Example (Cont')

6 PIs: BD, B'D', CD, B'C, AD, AB

 

2 EPIs:  $BD (m_5)$ ,  $B'D' (m_0)$

 

The remaining 4 PIs:  
 CD, B'C, AD, AB'

J.J. Shann 3-38

38

## Finding the Simplified Expression

### ■ Procedure for finding the simplified expression from the map: (SoP form)

- Determine all **PIs**.
  - The simplified expression is obtained from the logical sum of all the **EPIs** plus other **PIs** that may be needed to cover any **remaining minterms** not covered by the EPIs.
- There may be more than one expression that satisfied the simplification criteria.

J.J. Shann 3-39

39

## Example: p.3-33


### ■ Simplify the Boolean function

$$F(A,B,C,D) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$$


<Ans.>

6 PIs: BD, B'D', CD, B'C, AD, AB'

2 EPIs: BD, B'D'

 

 2 EPIs: **BD** ( $m_5$ ), **B'D'** ( $m_0$ )



4 PIs: **CD**, **B'C**, **AD**, **AB'**

EPIs: **BD**, **B'D'** →  $m_0, m_2, m_5, m_7, m_8, m_{10}, m_{13}, m_{15}$

⇒ Combine PIs that contains  $m_3, m_9, m_{11}$  (CD, B'C, AD, AB')

$$\begin{aligned} \Rightarrow F &= \mathbf{BD} + \mathbf{B'D'} + \mathbf{CD} + \mathbf{AD} \\ &= \mathbf{BD} + \mathbf{B'D'} + \mathbf{CD} + \mathbf{AB'} \\ &= \mathbf{BD} + \mathbf{B'D'} + \mathbf{B'C} + \mathbf{AD} \\ &= \mathbf{BD} + \mathbf{B'D'} + \mathbf{B'C} + \mathbf{AB'} \end{aligned}$$

$m_3, m_{11}$        $m_9, m_{11}$

J.J. Shann 3-40

40



## 補充資料 (Supplementary Materials)

### Five-Variable Map

*J.J. Shann*

41



### Five-Variable Map

- Five-variable map: 32 minterms  $\Rightarrow$  32 squares

$F(A, B, C, D, E)$

		CDE							
AB		000	001	011	010	110	111	101	100
		0	1	3	2	6	7	5	4
00									
01									
11									
10									

- Each square has 5 adjacent squares.

J.J. Shann 3-42

42





## Summary

- $n$ -variable map:  $2^n$  minterms  $\Rightarrow 2^n$  squares
  - Maps for more than 4 variables are not as simple to use:
    - Employ computer programs specifically written to facilitate the simplification of Boolean functions w/ a large # of variables.
- $\Rightarrow$  補充 Quine-McCluskey Method (p.3-58)

### Reference:

- Randy H. Katz & Gaetano Borriello, *Contemporary Logic Design*, Prentice Hall.

J.J. Shann 3-45

45



## 3-4

# Product of Sums (PoS) Simplification

*J.J. Shann*

46

## Product of Sums Simplification

### Approach 1: POS of $F$

- Simplified  $F'$  in the form of **sum of products**
- Apply DeMorgan's theorem  $F = (F')'$   
 $F'$ : sum of products  $\Rightarrow F = (F')'$ : product of sums

- E.g.: Simplify the Boolean function in POS:

$$F = \Sigma m(0, 4, 6)$$

$$\Rightarrow F' = \Sigma m(1, 2, 3, 5, 7)$$

$$= C + A'B \quad \dots \text{SoP}$$

$$\Rightarrow F = (C + A'B)'$$

$$= C' (A + B') \quad \dots \text{PoS}$$

		BC			
		00	01	11	10
A	0	0	1	3	2
	1	4	5	7	6

J.J. Shann 3-47

47

### Approach 2 (duality): POS of $F$

- combinations of **maxterms** ( it was minterms for SoP)
  - A **0** is marked in each **maxterm** that represents the function.
  - Find possible adjacent  $2^k$  squares and realize each set as a **sum (OR)** term, w/ variables being **complemented**.
- E.g.: for 4 variables

		CD			
		00	01	11	10
AB	00	$M_0$	$M_1$	$M_3$	$M_2$
	01	$M_4$	$M_5$	$M_7$	$M_6$
	11	$M_{12}$	$M_{13}$	$M_{15}$	$M_{14}$
	10	$M_8$	$M_9$	$M_{11}$	$M_{10}$

$$\begin{aligned}
 M_0 M_1 &= (A+B+C+\mathbf{D})(A+B+C+\mathbf{D}') \\
 &= (A+B+C) + (DD') \\
 &= A + B + C
 \end{aligned}$$

J.J. Shann 3-48

48



### Example 3.7

- Simplify the Boolean function in (a) SOP and (b) POS:  $F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$

<Ans.>

(a) SOP of  $F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$

CD \ AB	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

$$F = B'D' + B'C' + A'C'D$$

J.J. Shann 3-49

49

<Ans.>

(b) POS of  $F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$

Approach 1:

		$F$							$F'$			
		CD							CD			
AB		00	01	11	10		AB		00	01	11	10
00		1	1	0	1		00		0	0	1	0
01		0	1	0	0		01		1	0	1	1
11		0	0	0	0		11		1	1	1	1
10		1	1	0	1		10		0	0	1	0

$$F' = AB + CD + BD'$$

$$F = (F')' = (AB + CD + BD')' = (A'+B')(C'+D')(B'+D)$$

J.J. Shann 3-50

50

<Ans.>

(b) POS of  $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$

Approach 2: think in terms of maxterms

		$F$			
CD		00	01	11	10
AB	00	1	1	0	1
01	0	1	0	0	0
11	0	0	0	0	0
10	1	1	0	1	

$$F = \sum m(0,1,2,5,8,9,10) \\ = \prod M(3,4,6,7,11,12,13,14,15)$$



$$F = (A' + B')(C' + D')(B' + D)$$

J.J. Shann 3-51

51

– Gate implementation:

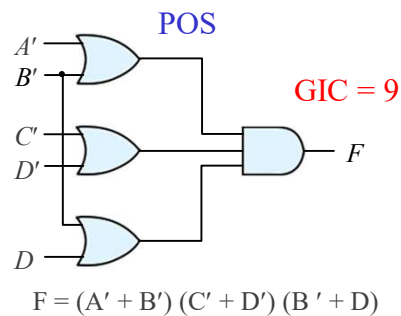 
Assumption: The input variables are directly available in their complement  $\Rightarrow$  Inverters are not needed.




- The implementation of a function in a **standard form** is said to be a **two-level implementation**.
- Determine which form will be best for a function.

J.J. Shann 3-52

52



## Example



■ Given the truth table of a function, simplify the function in (a) SOP and (b) POS.



$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

<Ans.>

$F(x, y, z) = \sum m(1, 3, 4, 6) = \prod M(0, 2, 5, 7)$


(a) SoP:  $F = x'z + xz'$

(b) PoS: Think in terms of maxterms  
 $F = (x + z)(x' + z')$

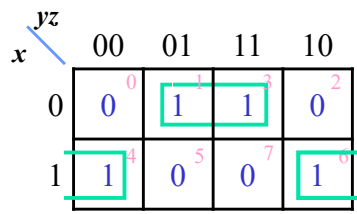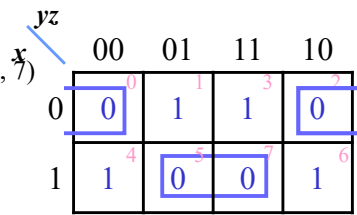J.J. Shann 3-53

53



## 3-5

---

# Don't-Care Conditions

*J.J. Shann*

54

## Don't-Care Conditions

### ■ *Don't care condition:*

- the unspecified minterms of a function
- is represented by an  $\times$
- E.g.: A 4-bit decimal code has 6 combinations which are not used.

### ■ *Incompletely specified function:*

- has unspecified outputs for some input combinations

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

\* 1010 ~ 1111 are not used and have no meaning.

J.J. Shann 3-55

55


## Simplification of an Incompletely Specified Function

### ■ Simplification of an incompletely specified function:

- When choosing adjacent squares to simplify the function in the map, the  $\times$ 's may be assumed to be either 0 or 1, whichever gives the simplest expression.
- An  $\times$  need not be used at all if it does not contribute to covering a larger area.


J.J. Shann 3-56

56



## Example 3.8

\* The outputs in a particular implementation of the function are only 0's and 1's.



■ Simplify the Boolean function  $F(w,x,y,z) = \Sigma m(1,3,7,11,15)$  which has the *don't-care* conditions  $d(w,x,y,z) = \Sigma m(0,2,5)$ .

<Ans.>

$\swarrow yz$ $\nwarrow wx$	00	01	11	10
00	×	1	1	×
01	0	×	1	0
11	0	0	1	0
10	0	0	1	0

$\swarrow yz$ $\nwarrow wx$	00	01	11	10
00	×	1	1	×
01	0	×	1	0
11	0	0	1	0
10	0	0	1	0

$\swarrow yz$ $\nwarrow wx$	00	01	11	10
00	×	1	1	×
01	0	×	1	0
11	0	0	1	0
10	0	0	1	0

(a) **SOP:**  $F(w,x,y,z) = yz + w'x' = \Sigma m(0,1,2,3,7,11,15)$   
 $F(w,x,y,z) = yz + w'z = \Sigma m(1,3,5,7,11,15)$

(b) **POS:**  $F(w,x,y,z) = z(w' + y) = \Sigma m(1,3,5,7,11,15)$  . Shann 3-57

57



# 補充資料 (Supplementary Materials)

---

## Quine-McCluskey Method & CAD Tools for Simplification

J.J. Shann

58

## A. Quine-McCluskey Method (for SOP)

- Tabular method to systematically find all PIs and a minimum cover of PIs for a function

### 1. Find all prime implicants ( $xy + xy' = x$ )

Implication  
Table

- (a) Fill Column 1 with **minterm** and **don't-care condition** indices.

Group by number of 1's.

- (b) Apply theorem  $xy + xy' = x$

Compare elements of **adjacent groups**.

Differ by one bit  $\Rightarrow$  Combine (eliminate a variable) and place in next column.

Mark the combined elements with a check ( $\checkmark$ ).

Repeat until no further combinations may be made.

Mark the uncombined elements with a star (\*)  $\Rightarrow$  PI.

### 2. Find the minimum cover of PIs $\Rightarrow$ simplified SOP

PI Chart

J.J. Shann 3-59

59

- Tabular method to systematically find all PIs and a minimum cover of PIs for a function

### 1. Find all prime implicants ( $xy + xy' = x$ )

### 2. Find the minimum cover of PIs

$\Rightarrow$  simplified SOP

PI Chart

- (a) Construct the Prime Implicant Chart

- (b) Find the **EPIs**

(\* EPIs must be in the set)

- (c) Select PIs to cover the remaining **minterms** if necessary

(\* Form the minimum set)

J.J. Shann 3-60

60

## Finding All Prime Implicants (1/4)

$$F(A,B,C,D) = \sum m(4, 5, 6, 8, 9, 10, 13) + \sum d(0, 7, 15)$$

### 1. Find all prime implicants:

#### Implication Table

(a) Fill Column 1 with *minterm* and *don't-care condition* indices.

\* Group by number of 1's.

0 1's

1 1's

2 1's

3 1's

4 1's

Implication Table	
Column 1	
0 0000	
4 0100	
8 1000	
5 0101	
6 0110	
9 1001	
10 1010	
7 0111	
13 1101	
15 1111	

J.J. Shann 3-61

61

## Finding All Prime Implicants (2/4)

(b) Apply theorem  $xy + xy' = x$  :

Compare elements of adjacent groups.

Differ by one bit

⇒ Combine (eliminate a variable) and place in next column.

Mark the combined elements with a check (✓).

Repeat until no further combinations may be made.

Group

0

1

2

3

4

Implication Table			
Column 1	Column 2		
0 0000 ✓	0,4 0-00		
8 1000 ✓	0,8 -000		
4 0100 ✓	4,5 010-		
8 1000 ✓	4,6 01-0		
5 0101 ✓	8,9 100-		
6 0110 ✓	8,10 10-0		
9 1001 ✓	5,7 01-1		
10 1010 ✓	5,13 -101		
7 0111 ✓	6,7 011-		
13 1101 ✓	9,13 1-01		
15 1111 ✓	7,15 -111		
	13,15 11-1		

J.J. Shann 3-62

62

## Finding All Prime Implicants (3/4)

(b) Apply theorem  $xy + xy' = x$  :

Compare elements of adjacent groups.

Differ by one bit

⇒ Combine (eliminate a variable) and place in next column.

Mark the combined elements with a check (✓).

Repeat until no further combinations may be made.

Mark the uncombined elements with a star (\*) ⇒ PI.

Implication Table				
	Column 1	Column 2	Column 3	
0	0000 ✓	0,4 0-00 *	4,5,6,7 01-- *	
4	0100 ✓	0,8 -000 *		
8	1000 ✓	4,5 010- ✓	5,7,13,15 -1-1 *	
5	0101 ✓	4,6 01-0 ✓		
6	0110 ✓	8,9 100- *		
9	1001 ✓	8,10 10-0 *		
10	1010 ✓	5,7 01-1 ✓		
7	0111 ✓	5,13 -101 ✓		
13	1101 ✓	6,7 011- ✓		
		9,13 1-01 *		
15	1111 ✓	7,15 -111 ✓		
		13,15 11-1 ✓		

J.J. Shann 3-63

63

## Finding All Prime Implicants (4/4)

Implication Table				
	Column 1	Column 2	Column 3	
0	0000 ✓	0,4 0-00 *	4,5,6,7 01-- *	
4	0100 ✓	0,8 -000 *		
8	1000 ✓	4,5 010- ✓	5,7,13,15 -1-1 *	
5	0101 ✓	4,6 01-0 ✓		
6	0110 ✓	8,9 100- *		
9	1001 ✓	8,10 10-0 *		
10	1010 ✓	5,7 01-1 ✓		
7	0111 ✓	5,13 -101 ✓		
13	1101 ✓	6,7 011- ✓		
		9,13 1-01 *		
15	1111 ✓	7,15 -111 ✓		
		13,15 11-1 ✓		

Prime Implicants:

0,4 0-00 → A' C' D'

0,8 -000 → B' C' D'

8,9 100- → A B' C'

8,10 10-0 → A B' D'

9,13 1-01 → A C' D

4,5,6,7 01-- → A' B

5,7,13,15 -1-1 → B D

J.J. Shann 3-64

64



## Finding the Minimum Cover (1/4)

2. Find the **smallest set of PIs** that **cover all the minterms**:

### Prime Implicant Chart

- (a) Construct the Prime Implicant Chart
- (b) Find the EPIs (\* EPIs must be in the set)
- (c) Select PIs to cover the remaining minterms if necessary (\* Form the minimum set)

J.J. Shann 3-66

66

## Finding the Minimum Cover (2/4)

(a) Construct the PI chart:

Rows = prime implicants

Columns = **minterms** only

(excludes don't-care conditions)

Place an "X" if minterm is covered by the PI.

$$F(A,B,C,D) = \Sigma m(4,5,6,8,9,10,13) + \Sigma d(0,7,15)$$

Prime Implicants:

$$0-00 = A' C' D' \quad 01-- = A' B$$

$$-000 = B' C' D' \quad -1-1 = B D$$

$$100- = A B' C'$$

$$10-0 = A B' D'$$

$$1-01 = A C' D$$

### Prime Implicant Chart

	4	5	6	8	9	10	13
0,4 (0-00)	X						
0,8 (-000)				X			
8,9 (100-)				X	X		
8,10 (10-0)				X		X	
9,13 (1-01)					X		X
4,5,6,7 (01--)	X	X	X				
5,7,13,15 (-1-1)		X					X

J.J. Shann 3-67

67

## Finding the Minimum Cover (3/4)

### (b) Find the EPIs

(\* EPIs must be in the set)

If a column has a single X,  
then the PI associated w/ the row  
is essential. (EPI)

It must appear in minimum cover.

2 EPIs:  $A B' D'$ ,  $A' B$

$$F = A B' D' + A' B + \dots$$

0,4 (0-00)

0,8 (-000)

8,9 (100-)

8,10 (10-0)

9,13 (1-01)

4,5,6,7 (01--)

5,7,13,15 (-1-1)

	4	5	6	8	9	10	13
0,4 (0-00)	X						
0,8 (-000)				X			
8,9 (100-)				X	X		
8,10 (10-0)				X		X	
9,13 (1-01)					X		X
4,5,6,7 (01--)	X	X	X				
5,7,13,15 (-1-1)		X					X

J.J. Shann 3-68

68

## Finding the Minimum Cover (4/4)

### (c) Select PIs to cover the remaining minterms if necessary

(\* Form the minimum set)

Eliminate all columns covered  
by EPI.

Find minimum set of rows that  
cover the remaining columns.

0,4 (0-00)

0,8 (-000)

8,9 (100-)

8,10 (10-0)

9,13 (1-01)

4,5,6,7 (01--)

5,7,13,15 (-1-1)

	4	5	6	8	9	10	13
0,4 (0-00)	X						
0,8 (-000)				X			
8,9 (100-)				X	X		
8,10 (10-0)				X		X	
9,13 (1-01)					X		X
4,5,6,7 (01--)	X	X	X				
5,7,13,15 (-1-1)		X					X

$$F = A B' D' + A' B + A C' D$$

J.J. Shann 3-69

69

## B. CAD Tools for Simplification

### ■ Problems of Quine-McCluskey Method:

- The # of PIs grows very quickly as the # of inputs increases.
- Finding a min set cover is a very difficult problem.
  - an NP-complete problem
  - There are not likely to be any efficient algorithms for solving it.

### ■ Espresso:

- a program for 2-level Boolean function minimization
- combines many of the best heuristic techniques developed
  - don't generate all PIs
  - judiciously select a subset of primes that still covers the minterms

J.J. Shann 3-71

71

## Espresso Inputs and Outputs

$$F(A,B,C,D) = \Sigma m(4,5,6,8,9,10,13) + d(0,7,15)$$

### Espresso Input

```
.i 4          # inputs
.o 1          # outputs
.ilb a b c d  input names
.ob f         output name
.p 10         # product terms
0100 1       A'BC'D'
0101 1       A'BC'D
0110 1       A'BCD'
1000 1       AB'C'D'
1001 1       AB'C'D
1010 1       AB'CD'
1101 1       ABC'D
0000 -       A'B'C'D' don't care
0111 -       A'BCD don't care
1111 -       ABCD don't care
.e           end of list
```

### Espresso Output

```
.i 4
.o 1
.ilb a b c d
.ob f
.p 3
1-01 1
10-0 1
01-- 1
.e
```

$$F = A' C' D + A' B' D' + A' B$$

J.J. Shann 3-72

72



## 補充資料 (Supplementary Materials)

---

# Multiple-Level Circuit Optimization

*J.J. Shann*

73



## Multiple-Level Circuit Optimization

---

- 2-level ckt optimization: simplified SoP, PoS
  - can reduce the cost of combinational logic ckts
  - 2-level ckt: minimal propagation delay
- Multi-level ckts:
  - ckts w/ more than 2 levels
  - There are often additional cost saving available
- Reference:
  - M. Morris Mano & Charles R. Kime, *Logic and Computer Design Fundamentals*, 3<sup>rd</sup> Edition, 2004, Pearson Prentice Hall. (§2-6)

J.J. Shann 3-74

74

## Transformations for Multiple-level Optimization

### ■ Multiple-level ckt optimization (simplification):

- is based on the use of a set of **transformations** that are applied in conjunction w/ cost evaluation to find a good, but not necessarily optimum solution.

*GIC, delay*

### ■ Transformations:

- **Factoring:** for *GIC* ↓
  - is finding a **factored form** from either a SoP or PoS expression for a function → **distributive law**
- **Elimination:** for *delay* ↓
  - function  $G$  in an expression for function  $F$  is replaced by the expression for  $G$  → **distributive law**

J.J. Shann 3-75

75

## A. Transformation for GIC Reduction (Factoring)

- E.g.:  $G = ABC + ABD + E + ACF + ADF$

<Ans.>

2-level implementation: gate-input cost = 17

Multi-level implementation: **distributive law**

$$G = \underline{ABC} + \underline{ABD} + E + \underline{ACF} + \underline{ADF} \quad (a) \rightarrow 17$$

$$= \underline{AB(C + D)} + E + \underline{AF(C + D)} \quad (b) \rightarrow 13$$

$$= (\underline{AB} + \underline{AF})(C + D) + E \quad (c) \rightarrow 12$$

$$= \underline{A(B + F)}(C + D) + E \quad (d) \rightarrow 9$$

Gate input count  
(GIC)

J.J. Shann 3-76

76

$G = ABC + ABD + E + ACF + ADF$  (a)  
 $= AB(C + D) + E + AF(C + D)$  (b)  
 $= (AB + AF)(C + D) + E$  (c)  
 $= A(B + F)(C + D) + E$  (d)

(a)  $G = ABC + ABD + E + ACF + ADF$

2 levels, GIC = 17

(b)  $G = AB(C + D) + E + A(C + D)F$

3 levels, GIC = 13

3 levels, GIC = 11

77

$G = ABC + ABD + E + ACF + ADF$  (a)  
 $= AB(C + D) + E + AF(C + D)$  (b)  
 $= (AB + AF)(C + D) + E$  (c)  
 $= A(B + F)(C + D) + E$  (d)

(c)  $G = (AB + AF)(C + D) + E$

4 levels, GIC = 12

(d)  $G = A(B + F)(C + D) + E$

3 levels, GIC = 9

Ckt	# Levels	GIC
(a)	2	17
(b)	3	13 (11)
(c)	4	12
(d)	3	9

78

J.J. Shann 3-78

## Example

- E.g.: Multilevel optimization transformations

$$G = \overline{A}\overline{C}E + \overline{A}\overline{C}F + \overline{A}\overline{D}E + \overline{A}\overline{D}F + BC\overline{D}\overline{E}\overline{F}$$

$$H = \overline{A}BCD + ABE + ABF + BCE + BCF$$

<Ans.>

GIC  
26

$$G = \overline{A}\overline{C}E + \overline{A}\overline{C}F + \overline{A}\overline{D}E + \overline{A}\overline{D}F + BC\overline{D}\overline{E}\overline{F}$$

$$= \overline{A}(\overline{C}E + \overline{C}F + \overline{D}E + \overline{D}F) + BC\overline{D}\overline{E}\overline{F}$$

$$= \overline{A}(\overline{C}(E + F) + \overline{D}(E + F)) + BC\overline{D}\overline{E}\overline{F}$$

18

$$= \overline{A}(\overline{C} + \overline{D})(E + F) + BC\overline{D}\overline{E}\overline{F}$$

$$= \overline{A}(\overline{C} + \overline{D})X_2 + BX_1\overline{E}\overline{F}$$

14

$$= \overline{A}\overline{X}_1X_2 + BX_1\overline{X}_2$$

$$\begin{aligned} X_1 &= CD \\ X_2 &= E + F \end{aligned}$$

substitution

J.J. Shann 3-79

79

(Cont'd)

$$G = \overline{A}\overline{X}_1X_2 + BX_1\overline{X}_2$$

$$X_1 = CD$$

$$X_2 = E + F$$

$$H = \overline{A}BCD + ABE + ABF + BCE + BCF$$

$$= B(\overline{A}CD + AE + AF + CE + CF)$$

$$= B(\overline{A}CD + \overline{A}(E + F) + C(E + F))$$

$$= B(\overline{A}(CD) + (A + C)(E + F))$$

$$= B(\overline{A}X_1 + (A + C)X_2)$$

⇒

$$G = \overline{A}\overline{X}_1X_2 + BX_1\overline{X}_2$$


$$H = B(\overline{A}X_1 + (A + C)X_2)$$

$$X_1 = CD$$

$$X_2 = E + F$$

J.J. Shann 3-80

80

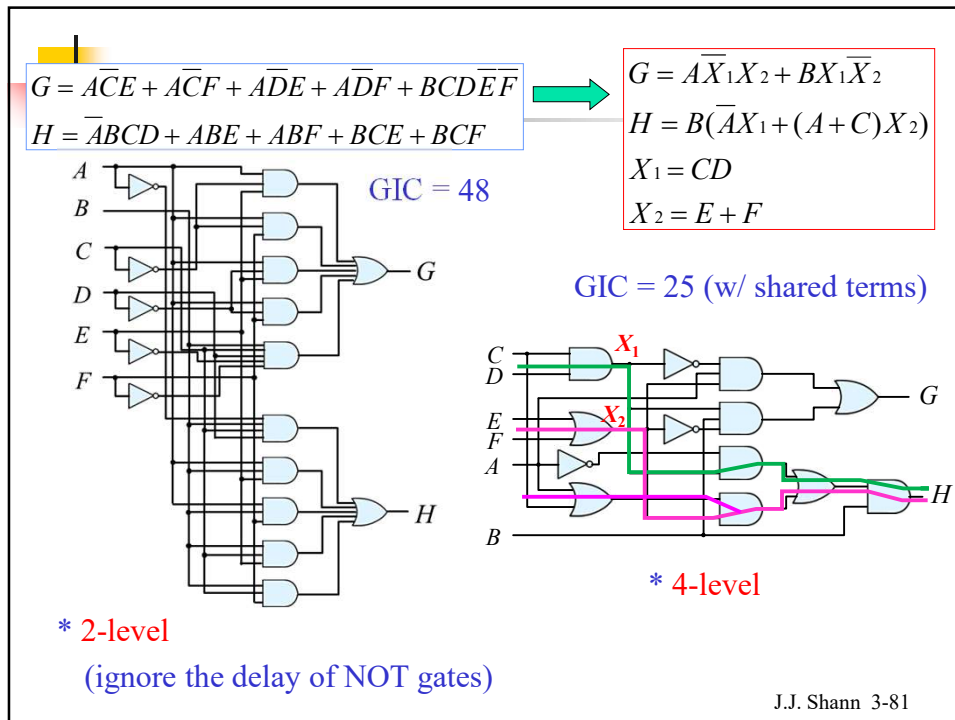

81

## 3-6

---

# NAND & NOR Implementation

*J.J. Shann*

87



## NAND & NOR Implementation

### ■ NAND & NOR gates:

- are easier to fabricate w/ electronic components.
- are the basic gates used in all IC digital logic families.
- have the **universal property**:
  - Any Boolean function can be implemented w/ NAND (NOR) gates only.

### ■ Boolean function in terms of AND, OR, NOT ⇒ equivalent NAND (NOR) logic diagram


J.J. Shann 3-88

88

## A. NAND Circuits
 
### ■ Universal property of the NAND gate:



- The logical operations of AND, OR, NOT can be obtained w/ NAND gates only.



J.J. Shann 3-89

89

■ Two graphic symbols for NAND gate:

  

■ Implementation of a combinational ckt w/ NAND gates:

- Obtain the simplified Boolean functions in terms of **AND**, **OR**, **NOT**.
- Convert the function to **NAND** logic.

J.J. Shann 3-90





90

## Two-Level NAND Implementation

■ Two-level NAND implementation:

Sum of products (AND-OR)  $\Rightarrow$  NAND-NAND

■ Example:  $F = AB + CD$

    


$$(a) \rightarrow (c): F = AB + CD = [(AB + CD)']' = [(AB)' (CD)']'$$

$$(c) \rightarrow (a): F = [(AB)' (CD)']' = AB + CD$$

J.J. Shann 3-91

91

### Example 3.9

 


- Implement the following Boolean function w/ NAND gates:  $F(x,y,z) = \Sigma(1,2,3,4,5,7)$

<Ans.>


- i. Simplify the function in **SOP**:

$x \backslash yz$	00	01	11	10
0		1	1	1
1	1	1	1	

$$F = xy' + x'y + z$$

 


 
- ii. Convert the function to NAND logic:



J.J. Shann 3-92

92

$$F = xy' + x'y + z$$

  

- Procedure of implementing a Boolean function w/ two-level NAND gates:

- Simplify the function and express it in **sum of products**.
- Draw a NAND gate for each **product term** of the expression that has at least two literals. The inputs to each NAND gate are the literals of the term.  
→ 1<sup>st</sup> level
- Draw a single NAND gate (using the AND-invert or the invert-OR graphic symbol), w/ inputs coming from outputs of 1<sup>st</sup> level gates. → 2<sup>nd</sup> level
- A term w/ a single literal requires an inverter in the 1<sup>st</sup> level or may be complemented and applied as an input of the 2<sup>nd</sup>-level NAND gate.


J.J. Shann 3-93

93

## Multilevel NAND Circuits

- Standard form of Boolean function  
 $\Rightarrow$  2-level implementation
- Nonstandard form  $\Rightarrow$  Multilevel circuit

– E.g.:  $F = A(CD + B) + BC'$

 

J.J. Shann 3-94

94

## Procedure for obtaining a multilevel NAND diagram:


- From a given Boolean expression, draw the logic diagram w/ AND, OR, and invert gates.
  - Assumption: Both the normal and complement inputs are available.
- Convert all AND gates to NAND gates w/ AND-invert graphic symbol.
- Convert all OR gates to NAND gates w/ invert-OR graphic symbols.
- Check all the bubbles in the diagram. For every bubble that is not compensated by another small circle along the same line, insert an inverter (one-input NAND gate) or complement the input literal.

J.J. Shann 3-95


95

## Example

AND

 


OR

 

- Implement the multilevel Boolean function using NAND gates:  $F = (AB' + A'B)(C + D')$

<Ans.>

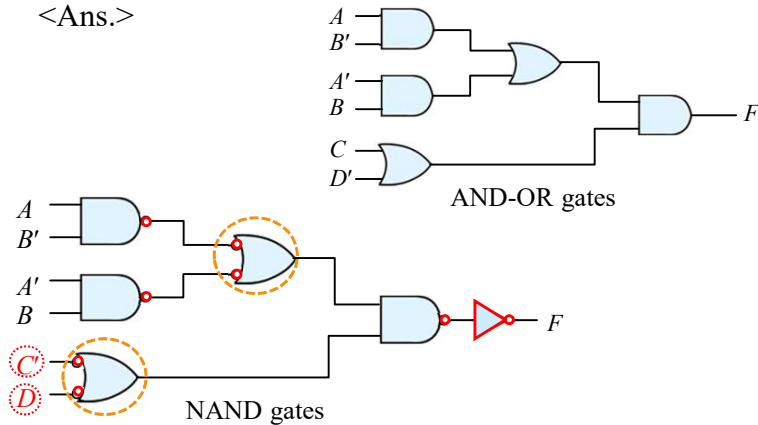


J.J. Shann 3-96

96
 
## B. NOR Implementation


- NOR operation: the dual of NAND operation
  - All procedures and rules for NOR logic are the dual of those developed for NAND logic.
- Universal property of the NOR gate:
  - The logical operations of AND, OR, NOT can be obtained w/ NOR gates only.




J.J. Shann 3-97

97

■ Two graphic symbols for NOR gate:

 

OR-invert

 

Invert-AND

■ Implementation of a combinational ckt w/ NOR gates:

- i. Obtain the simplified Boolean functions in terms of **AND**, **OR**, **NOT**.
- ii. Convert the function to **NOR** logic.

J.J. Shann 3-98

98



## Two-Level NOR Implementation

■ Two-level NOR implementation:


Product of sums (OR-AND)  $\Rightarrow$  NOR-NOR

■ Procedure of implementing a Boolean function w/ two-level NOR gates:

  
1. Simplify the function and express it in **product of sums**.
2. Draw the OR-AND diagram of the POS expression.
3. **OR** gates  $\rightarrow$  NOR gates w/ **OR-invert** graphic symbols.  
**AND** gate  $\rightarrow$  NOR gate w/ **invert-AND** graphic symbol.
4. A **single literal term** going into the 2<sup>nd</sup>-level gate must be **complemented**



99

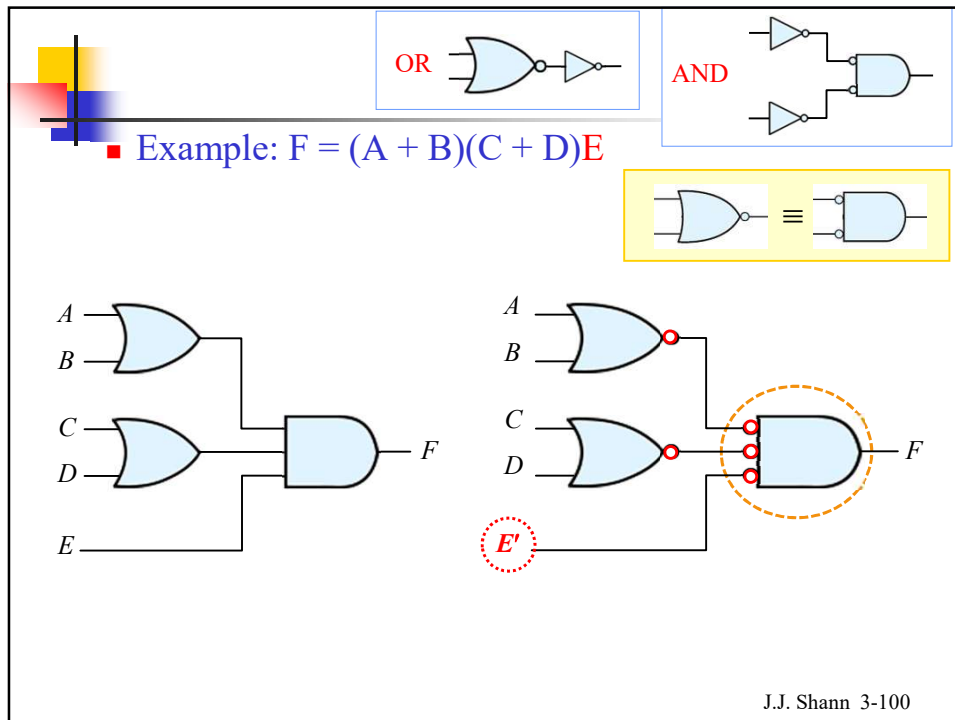

100

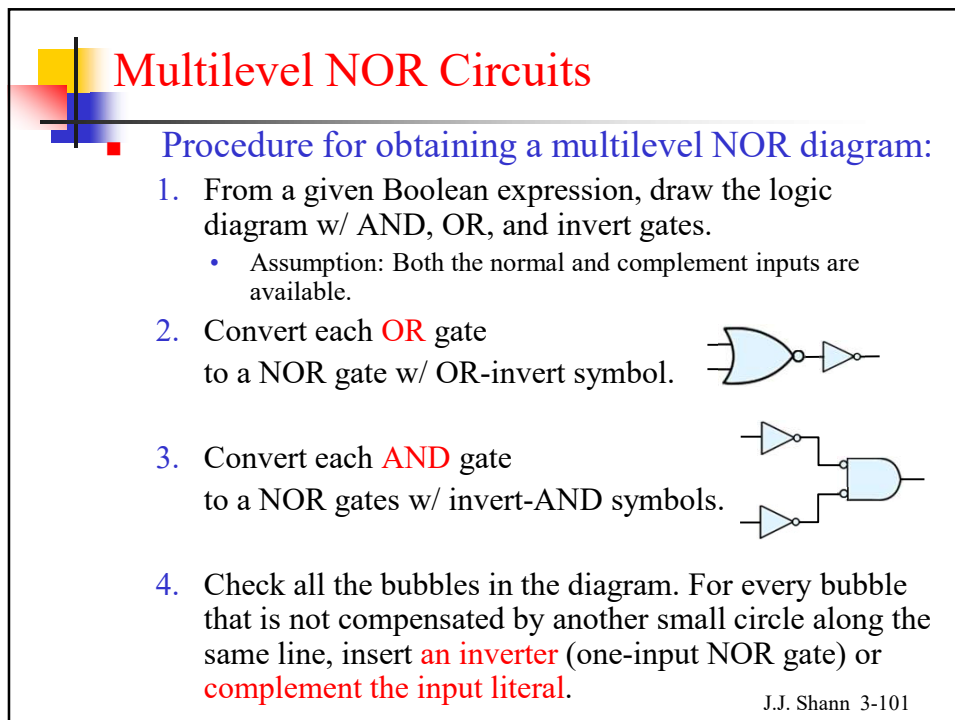

101

## Example

OR

AND

■ Implement the multilevel Boolean function using NOR gates:  $F = (AB' + A'B)(C + D')$

<Ans.>

AND-OR gates

NOR gates

J.J. Shann 3-102

102

## 3-7

# Other Two-Level Implementations

*J.J. Shann*

103



## Other Two-Level Implementations

- The types of gates most often found in ICs are **NAND and NOR**.
  - NAND and NOR logic implementations are the most important from a practical point of view.
- **Wired logic:**
  - Some NAND or NOR gates allow the possibility of a wire connection b/t the outputs of two gates to provide a specific logic function.
  - E.g.: Wired-AND logic  
Wired-OR logic

J.J. Shann 3-104

104

## Wired Logic

\* The wired-logic gate is not a physical gate.


### ■ Wired-AND logic:

- E.g.: open-collector TTL NAND gates

$$F = (AB)' (CD)'$$

$$= (AB + CD)'$$

 **NAND-AND  $\Rightarrow$  AND-OR-INVERT (AOI) function**




### ■ Wired-OR logic:

- E.g.: ECL NOR gates

$$F = (A + B)' + (C + D)'$$

$$= [(A + B) (C + D)]'$$

 **NOR-OR  $\Rightarrow$  OR-AND-INVERT (OAI) function**



J.J. Shann 3-105

105

## 2-Level Combinations of Gates

### 2-level combinations of gates:

AND, OR, NAND, NOR  $\Rightarrow$  16

#### – Degenerate forms: 8

(degenerate to a single operation; 2-level  $\rightarrow$  1-level)

AND-AND	OR-OR	NAND-OR	NOR-AND
AND-NAND	OR-NOR	NAND-NOR	NOR-NAND

#### – Nondegenerate forms: 8

AND-OR	OR-AND	NAND-NAND	NOR-NOR
<b>NAND-AND</b>	<b>NOR-OR</b>	AND-NOR	OR-NAND

> AND-OR & NAND-NAND  $\Leftrightarrow$  sum of products (AO)

> OR-AND & NOR-NOR  $\Leftrightarrow$  product of sums (OA)

> **NAND-AND** **NOR-OR** **AND-NOR** **OR-NAND**  $\Leftrightarrow$  ?

AOI (A.)

OAI (B.)

J.J. Shann 3-106

106


## A. AND-OR-Invert (AOI) Implementation (AND-NOR & NAND-AND)

### AND-OR-Invert: inversion of SoP

#### – Simplify $F'$ in SoP

– E.g.:  $F' = AB + CD + E$  (sum of products)

$$\Rightarrow F = (AB + CD + E)'$$

 

AND-OR-Invert  $\Leftrightarrow$  AND-NOR  $\Leftrightarrow$  NAND-AND


J.J. Shann 3-107

107


## B. OR-AND-Invert (OAI) Implementation (OR-NAND & NOR-OR)
 
### ■ OR-AND-Invert: inversion of PoS


- Simplify  $F'$  in PoS
- E.g.:  $F' = (A + B)(C + D)E$  (product of sums)  
 $\Rightarrow F = [(A + B)(C + D)E]'$



OR-NAND

 

OR-NAND

 

NOR-OR

OR-AND-Invert  $\Leftrightarrow$  OR-NAND  $\Leftrightarrow$  NOR-OR

J.J. Shann 3-108

108

## C. Tabular Summary

### ■ Implementation w/ other 2-level forms:

Implementation with Other Two-Level Forms

Equivalent Nondegenerate Form		Implements the Function	Simplify $F'$ into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	SoP $F$
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	PoS $F$

\*Form (b) requires an inverter for a single literal term.

J.J. Shann 3-109

109

### Example 3.10

- Implement the following function w/ AND-NOR, NAND-AND, OR-NAND, NOR-OR 2-level forms:

$$F(x, y, z) = \Sigma(0, 6)$$

<Ans.>

		$yz$			
		00	01	11	10
$x$	0	1 <sup>0</sup>	0 <sup>1</sup>	0 <sup>3</sup>	0 <sup>2</sup>
	1	0 <sup>4</sup>	0 <sup>5</sup>	0 <sup>7</sup>	1 <sup>6</sup>

SoP of  $F = x'y'z' + xyz'$

PoS of  $F = (x + y')(x' + y)z'$

SoP of  $F' = x'y + xy' + z$

PoS of  $F' = (x + y + z)(x' + y' + z)$

J.J. Shann 3-110

110

SoP of  $F = x'y'z' + xyz'$

PoS of  $F = (x + y')(x' + y)z'$



SoP of  $F' = x'y + xy' + z$

PoS of  $F' = (x + y + z)(x' + y' + z)$

– AND-NOR & NAND-AND implementations: AOI


Simplify  $F'$  in SoP: SoP of  $F' = x'y + xy' + z$
  
$$\Rightarrow F = (x'y + xy' + z)' \quad \dots \text{AOI}$$




J.J. Shann 3-111

111




SoP of  $F = x'y'z' + xyz'$   
 PoS of  $F = (x + y')(x' + y)z'$   
 SoP of  $F' = x'y + xy' + z$   
**PoS of  $F' = (x + y + z)(x' + y' + z)$**




– **OR-NAND & NOR-OR** implementations: **OAI**

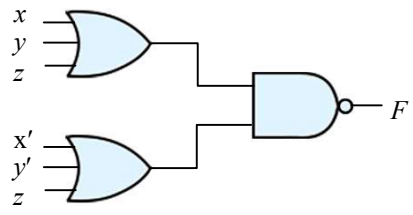Simplify **F'** in **PoS**: PoS of  $F' = (x + y + z)(x' + y' + z)$   
 $\Rightarrow F = [(x + y + z)(x' + y' + z)]' \dots \text{OAI}$




OR-NAND

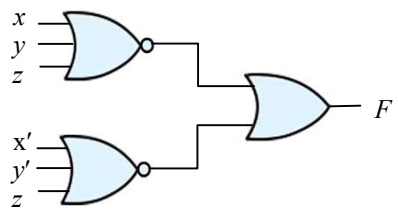

NOR-OR

J.J. Shann 3-112

112



## 3-8

# Exclusive-OR Function

*J.J. Shann*

113

## Exclusive-OR Function

- Exclusive-OR: XOR,  $\oplus$

$$x \oplus y = xy' + x'y$$

– is equal to 1 if only  $x = 1$  or if only  $y = 1$ , but not both.

- Exclusive-NOR: XNOR, equivalence

$$(x \oplus y)' = xy + x'y'$$

– is equal to 1 if both  $x$  and  $y$  are equal to 1 or if both are equal to 0.

\* Two-variable XOR & XNOR are the complement to each other.

- They are particularly useful in arithmetic operations and error-detection and correction ckts.

J.J. Shann 3-114

114

## Properties of XOR

$$x \oplus y = xy' + x'y$$

- Identities:

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$x \oplus x = 0$$

$$x \oplus x' = 1$$

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$

- Commutativity and associativity:

$$A \oplus B = B \oplus A$$

$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$


$\Rightarrow$  XOR gates w/ three or more inputs

J.J. Shann 3-115

115
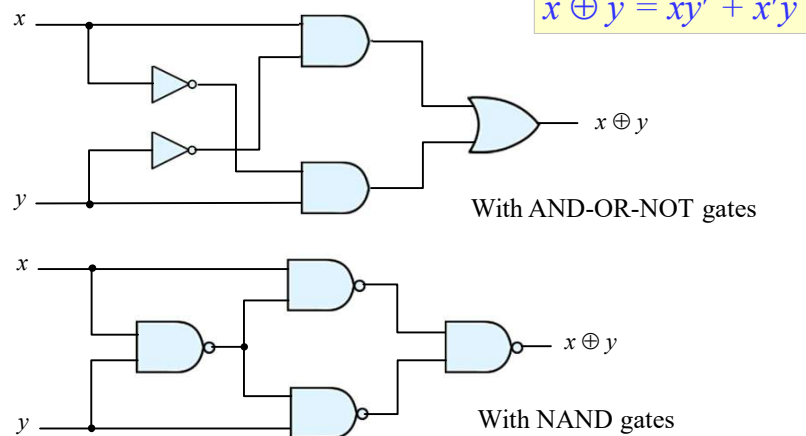
## Implementations of XOR function

- XOR function is usually constructed w/ other types of gates:



J.J. Shann 3-116

116

## Odd Function

$$x \oplus y = xy' + x'y$$

- Multiple-variable XOR operation: odd function
  - equal to 1 if the input variables have an **odd** # of 1's
- E.g.: 3-variable XOR

$$\begin{aligned} A \oplus B \oplus C &= (A \oplus B)C' + (A \oplus B)'C \\ &= (AB' + A'B)C' + (AB + A'B')C \\ &= AB'C' + A'BC' + ABC + A'B'C \\ &= \Sigma(1, 2, 4, 7) \end{aligned}$$

⇒ is equal to 1 if only one variable is equal to 1 or if all three variables are equal to 1.

		BC			
		00	01	11	10
A	0	0	1	3	2
	1	4	5	7	6

J.J. Shann 3-117

117

■ E.g.: 4-variable XOR

$$\begin{aligned}
 & A \oplus B \oplus C \oplus D \\
 &= (AB' + A'B) \oplus (CD' + C'D) \\
 &= (AB' + A'B)(CD' + C'D)' \\
 &\quad + (AB' + A'B)'(CD' + C'D) \\
 &= (AB' + A'B)(CD + C'D') \\
 &\quad + (AB + A'B')(CD' + C'D) \\
 &= \Sigma(1, 2, 4, 7, 8, 11, 13, 14)
 \end{aligned}$$

		CD			
		00	01	11	10
AB	00		1		1
	01	1		1	
	11		1		1
	10	1		1	

- An  $n$ -variable XOR function is defined as the logical sum of the  $2^n/2$  minterms whose binary numerical values have an odd # of 1's.

J.J. Shann 3-118


118

Even Function

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$

- XNOR is commutative and associative
 
$$\begin{aligned}
 (A \oplus B)' &= (B \oplus A)' \\
 [(A \oplus B)' \oplus C]' &= [A \oplus (B \oplus C)]' \\
 &= A \oplus B \oplus C \\
 &\neq (A \oplus B \oplus C)'
 \end{aligned}$$



- Modifying the definition of multiple-variable XNOR operation: even function

— equal to 1 if the input variables have an even # of 1's

J.J. Shann 3-119

119



■ E.g.: 3-variable XNOR

XOR:  $A \oplus B \oplus C = \Sigma(1,2,4,7)$

XNOR:  $(A \oplus B \oplus C)' = \Sigma(0,3,5,6)$

A \ BC	BC			
	00	01	11	10
0	0	1 <sup>1</sup>		1 <sup>2</sup>
1	1 <sup>4</sup>		1 <sup>7</sup>	

Odd function  $F = A \oplus B \oplus C$

A \ BC	BC			
	00	01	11	10
0	1 <sup>0</sup>		1 <sup>3</sup>	
1		1 <sup>5</sup>		1 <sup>6</sup>

Even function  $F = (A \oplus B \oplus C)'$

J.J. Shann 3-120

120

■ E.g.: 4-variable XNOR

XOR:  $A \oplus B \oplus C \oplus D = \Sigma(1, 2, 4, 7, 8, 11, 13, 14)$

XNOR:  $(A \oplus B \oplus C \oplus D)' = \Sigma(0, 3, 5, 6, 9, 10, 12, 15)$

AB \ CD	CD			
	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

Odd function  $F = A \oplus B \oplus C \oplus D$

AB \ CD	CD			
	00	01	11	10
00	1		1	
01		1		1
11	1		1	
10		1		1

Even function  $F = (A \oplus B \oplus C \oplus D)'$


- An  $n$ -variable **XNOR** function is defined as the logical sum of the  $2^n/2$  minterms whose binary numerical values have an **even** # of 1's.

J.J. Shann 3-121

121

## Logic Diagram of Odd & Even Functions

- Logic diagram of odd & even functions:

 


J.J. Shann 3-122

122
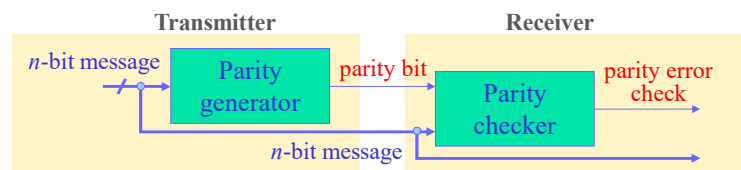
## Parity Generation & Checking




- Error-detection and correction codes: (§1-7, §7-4)
- Parity bit:
  - detecting errors during transmission of binary information.
  - is an extra bit included w/ a binary message to make the # of 1's either odd or even.
  - The message, including the parity bit, is transmitted and then checked at the receiving end for errors.
  - Parity generator:** generates the parity bit in the transmitter
  - Parity checker:** checks the parity in the receiver



123
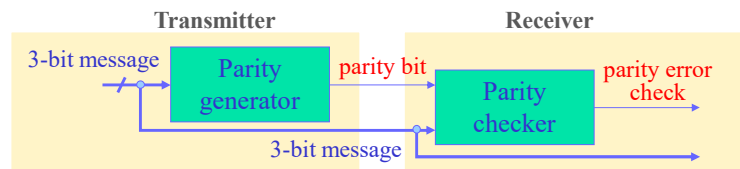
## Example

- Consider a 3-bit message to be transmitted together w/ an even parity bit.



J.J. Shann 3-124

124

Even-parity generator:

3-bit msg x y z	Parity Bit P
0 0 0	
0 0 1	
0 1 0	
0 1 1	
1 0 0	
1 0 1	
1 1 0	
1 1 1	

$$P = x \oplus y \oplus z$$


Even-parity checker:  
C = 1 if error occurs

4-bit received x y z P	Error check C
0 0 0 0	
0 0 0 1	
0 0 1 0	
0 0 1 1	
0 1 0 0	
0 1 0 1	
0 1 1 0	
0 1 1 1	
1 0 0 0	
1 0 0 1	
1 0 1 0	
1 0 1 1	
1 1 0 0	
1 1 0 1	
1 1 1 0	
1 1 1 1	

$$C = x \oplus y \oplus z \oplus P$$

J.J. Shann 3-125

125

 

126

**3-9**

# Hardware Description Language (HDL)

J.J. Shann

127

## Hardware Description Language (HDL)

### ■ HDL:

- is a language that describes the hardware structure and behavior of digital systems in a textual form.
- Can be used to represent logic diagrams, Boolean expressions, and other more complex digital ckt.

### ■ Two applications of HDL processing:


- Logic simulation:
  - the representation of the structure and behavior of a digital logic system through the use of a computer.
- Logic synthesis:
  - the process of deriving a list of components and their interconnections (*netlist*) from the model of a digital system described in HDL.

J.J. Shann 3-128

128

## Module Declaration

### ■ HDL Example:

 

//Verilog model of circuit of Figure 3.37

```
module Simple_Circuit (A, B, C, D, E);
    output D, E;
    input A, B, C;
    wire w1;

    and G1 (w1, A, B); //Optional gate instance name
    not G2 (E, C);
    or G3 (D, w1, E);
endmodule
```

J.J. Shann 3-129

129



## Chapter Summary

- Minimization of Boolean function:
  - Algebraic manipulation: literal minimization (Ch2)
  - Map method: gate-level minimization (§3-2~3-5)
    - SoP simplification & PoS simplification
    - Don't-care conditions
  - Tabular method: Quine-McCluskey method (補充資料)
- Multiple-Level Circuit Optimization (補充資料)
- NAND and NOR Implementation
- Other two-level implementation
- XOR and XNOR Functions
- Hardware Description Language (HDL)

J.J. Shann 3-130